

1. A bipolar junction transistor is biased at $I_C = 2 \text{ mA}$ and $T = 300^\circ\text{K}$. The transistor parameters are $\beta = 100$, $V_A = 100 \text{ V}$.
 - (a) Sketch its low frequency hybrid- π equivalent circuit and determine the transconductance, base input resistance and collector output resistance. (4%)
 - (b) Based on your hybrid- π circuit, determine the h-parameters: h_{ic} , h_{re} , h_{fe} and h_{oc} . (4%)
 - (c) Repeat (b) when a resistor $r_{cb} = 1 \text{ M}\Omega$ is connected between base and collector. (8%)

2. A MOSFET with parameters $k_n = 0.5 \text{ mA/V}^2$, $V_{TN} = 1 \text{ V}$ is used in the circuit of Fig. 1. The component values are $V^+ = -V^- = 10 \text{ V}$, $I_Q = 2 \text{ mA}$, $C_1 = C_2 = \infty$, $R_i = 500 \Omega$, $R_D = 2.5 \text{ k}\Omega$.
 - (a) Find the dc voltage of source V_s . (4%)
 - (b) Sketch the small signal equivalent circuit. (4%)
 - (c) Calculate the values R_{in} and V_o/V_i . (6%)

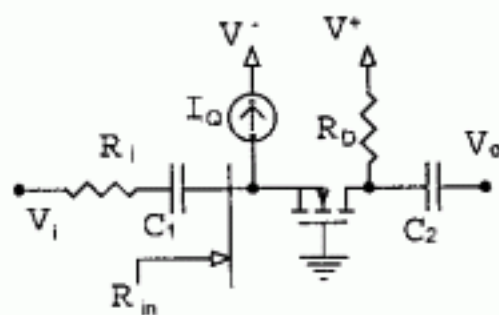


Fig. 1

3. A common source equivalent circuit is shown Fig. 2, the transistor transconductance is $g_m = 3 \text{ mA/V}$. (a) Calculate the equivalent Miller capacitance. (b) Determine the upper 3dB frequency (in Hz) for the small signal voltage gain. (10%)

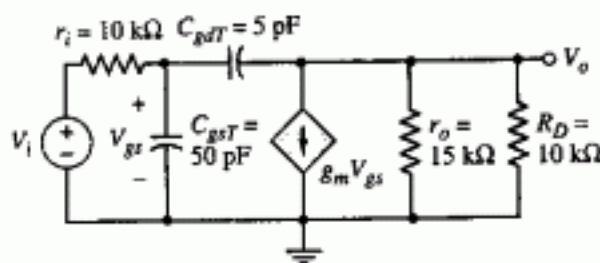


Fig. 2

4. Consider the current source shown in Fig. 3, with transistor parameters $\mu_n C_{ox} = 40 \mu A/V^2$, $V_{TH} = 1 V$, and $\lambda = 0$. Let $V^+ = 5 V$, $V^- = 0$, $V_{GS2} = 1.85 V$. Design the circuit such that $I_{REF} = 0.25 mA$, and $I_O = 0.1 mA$. (10%)

5. The transistors in the circuit of Fig. 4 have $\beta = 100$, $V_{BE(on)} = 0.7 V$, and $V_A = 100 V$. Determine the differential- and common-mode input resistance, R_{id} and R_{icm} . Assume thermal voltage $V_T = 25 mV$. (15%)

6. Sketch and carefully label v_o for each of the circuits described in Fig. 5, given the power supplies are $\pm 10 V$, and $v_{in} = 1 \sin wt$ volts.

(a) The circuit has the form given in Fig. 1 with $R_f = 5 k\Omega$ and $R_2 = 1 k\Omega$. In addition, an ideal diode is connected in series with R_2 (cathode on the left). (5%)

(b) The circuit is the same as in part (a) except that the diode is connected in series with R_f . (5%)

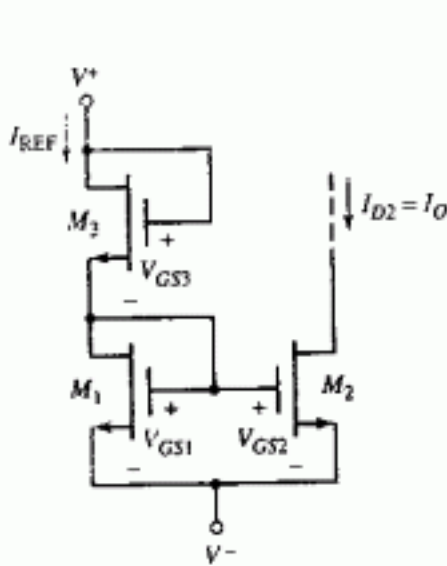


Fig. 3

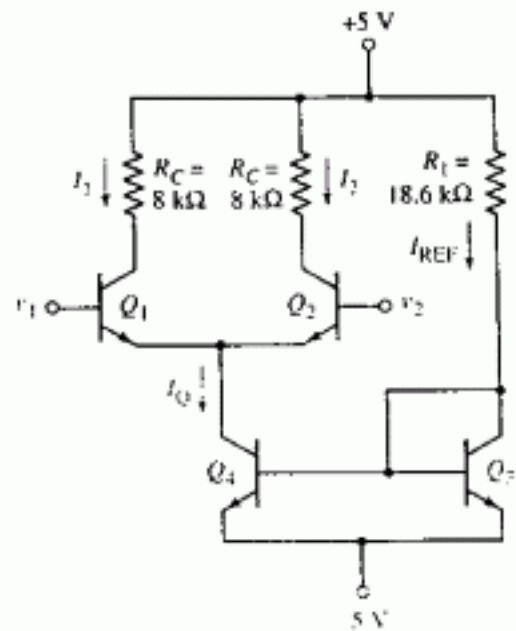


Fig. 4

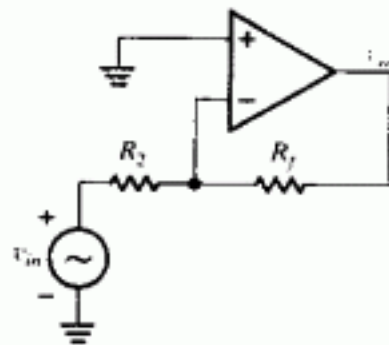


Fig. 5

7. An inverting-style op amp circuit is constructed with $R_2 = 10 \text{ k}\Omega$ and R_f replaced by an inductor $L = 100 \text{ mH}$. Determine the stability of this circuit. Assuming that the op amp has the A_{OL} gain-phase characteristics as shown in Fig.6. (10%)
8. The circuit illustrated in Fig. 7 is known as a Wien bridge oscillator.
 - (a) Determine the frequency of oscillation. (5%)
 - (b) Find the op amp closed-loop gain needed to just make this circuit oscillate. (5%)
 - (c) Plot the gain-phase characteristics of the feedback network. (5%)

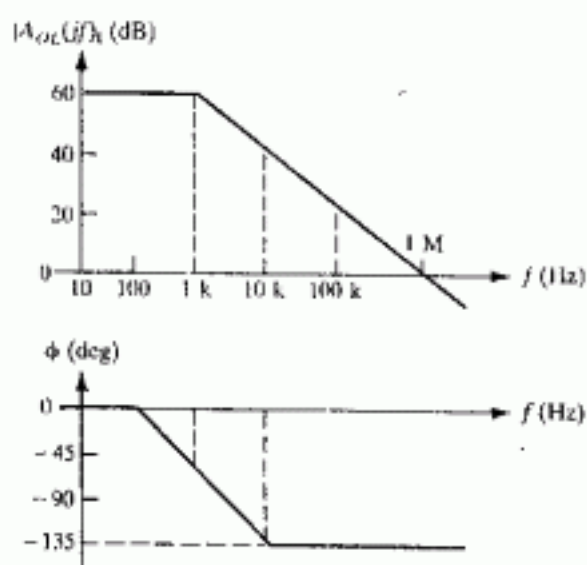


Fig. 6

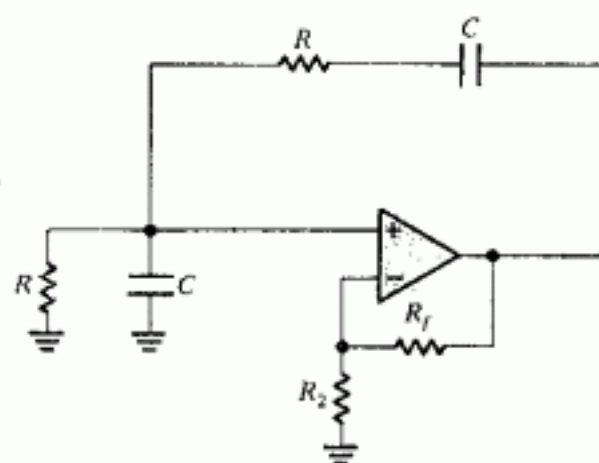


Fig. 7