


Chapter 5 Faraday's Law Transient Process

5.1 Faraday's Law of Induction

5.2 Two Kinds of Electromotance

5.3 Mutual Inductance and Self-Inductance

5.4 Transient Process

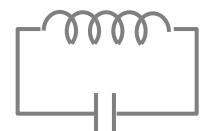


5.4 Transient Process

◆ The R-L Circuit

* Switch up

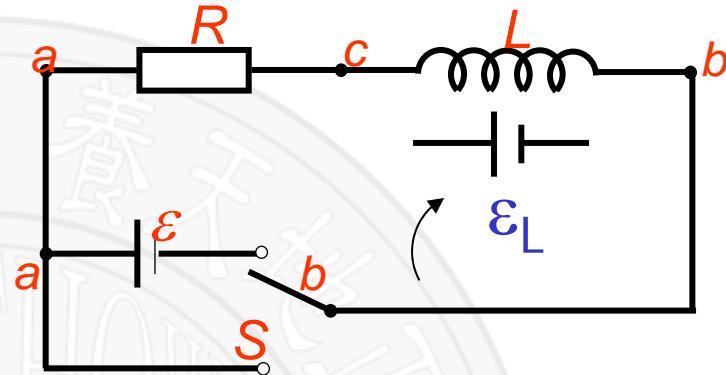↗ i increases, self-induction
emf opposes the increase



Show RL-Circuit


↗ According to Kirchhoff's Second Law, we get

$$iR + L \frac{di}{dt} - \varepsilon = 0$$

↗ A differential equation

$$\frac{di}{(\varepsilon / R) - i} = \frac{R}{L} dt$$

variables separation

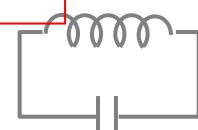

5.4 Transient Process

◆ The R-L Circuit

* Switch up

$$\int_0^i \frac{di}{(\varepsilon / R) - i} = \int_0^t \frac{R}{L} dt$$



$$\frac{\varepsilon}{R} - i = \frac{\varepsilon}{R} e^{-\frac{R}{L}t}$$

$$i = \frac{\varepsilon}{R} (1 - e^{-\frac{R}{L}t}) = I_0 (1 - e^{-\frac{R}{L}t})$$

▲ Time constant $\tau = \frac{L}{R}$

decay constant or relaxation time

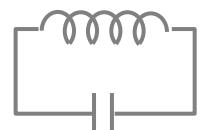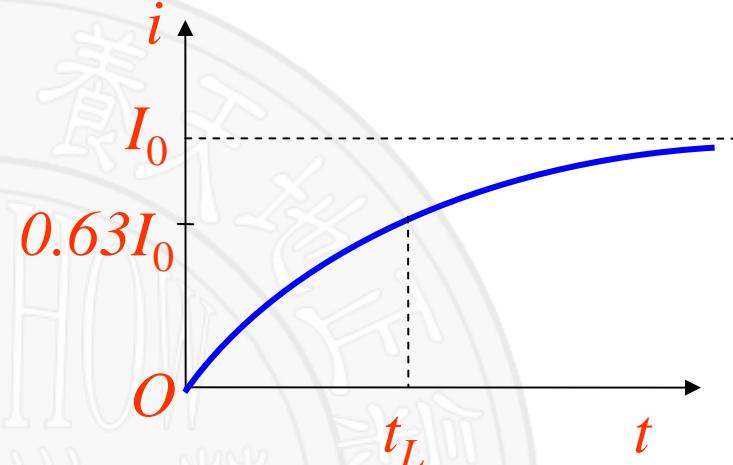At a time t equal to L/R the current has risen to $(1-1/e)$ or about 63% of its final value.



5.4 Transient Process

❖ The R-L Circuit

- ▲ Half-life time
 - The time required for the current to reach half its final value


$$e^{-(R/L)t} = \frac{1}{2}$$

$$T_{\frac{1}{2}} = \frac{L}{R} \ln 2$$

- time unit

$$\tau = \frac{L}{R}$$

L:H, 1H=1Ω·s, τ:s

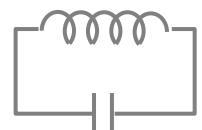

5.4 Transient Process

◆ The R-L Circuit



* Switch down

▲ i decreases, self-induction emf opposes the decrease

▲ According to Kirchhoff's Second Law, we get

$$iR + L \frac{di}{dt} = 0$$

▲ A differential equation

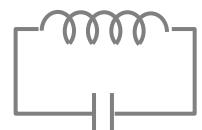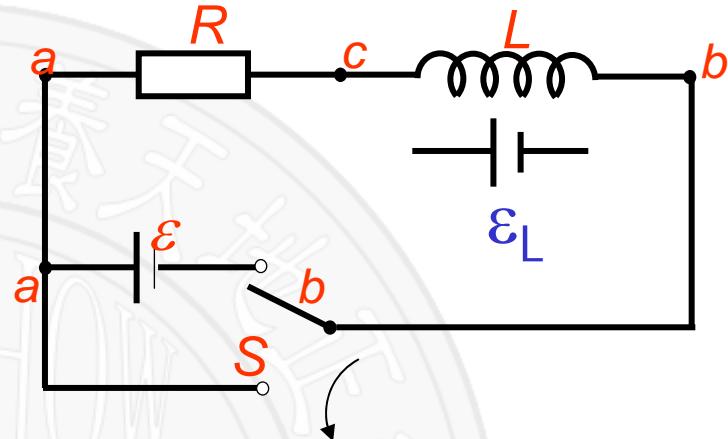

5.4 Transient Process

◆ The R-L Circuit

* Switch down



$$\frac{di}{i} = -\frac{R}{L} dt$$

$$\int_{I_0}^i \frac{di}{i} = \int_0^t -\frac{R}{L} dt$$

$$\ln\left(\frac{i}{I_0}\right) = -\frac{R}{L} t$$

$$i = I_0 e^{-\frac{R}{L}t} = \frac{\mathcal{E}}{R} e^{-\frac{R}{L}t}$$

When $t=L/R$, $i=37\%$ of I_0

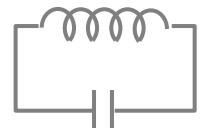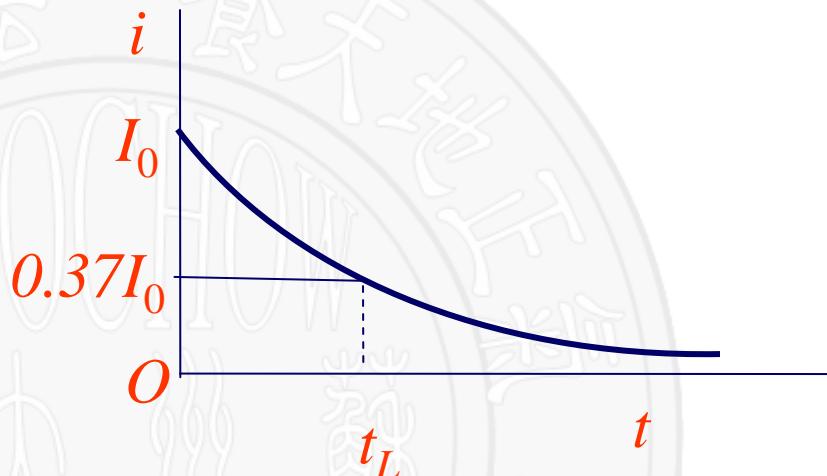

5.4 Transient Process

◆ The R-C Circuit

* Switch Up: charging


According to Kirchhoff's Second Law, we get

$$iR + \frac{q}{C} - \varepsilon = 0$$


$$i = \frac{dq}{dt}$$

differential equation
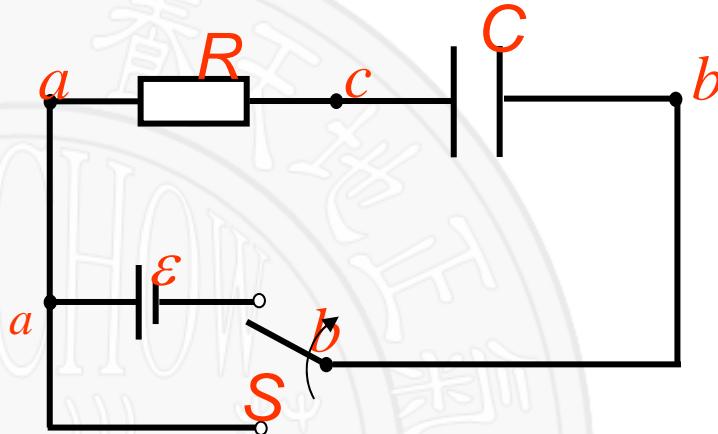
$$\frac{d q}{d t} = \frac{\varepsilon}{R} - \frac{q}{RC}$$



Show RC-Circuit

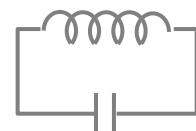

5.4 Transient Process

◆ The R-C Circuit

* Switch Up: charging




$$\frac{dq}{\varepsilon C - q} = \frac{dt}{RC}$$

$$\int_0^q \frac{dq}{\varepsilon C - q} = \int_0^t \frac{dt}{RC}$$

$$-\ln \frac{\varepsilon C - q}{\varepsilon C} = \frac{t}{RC}$$

$$q = \varepsilon C (1 - e^{-\frac{t}{RC}}) = Q_f (1 - e^{-\frac{t}{RC}})$$
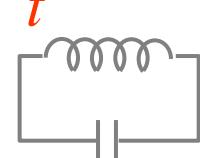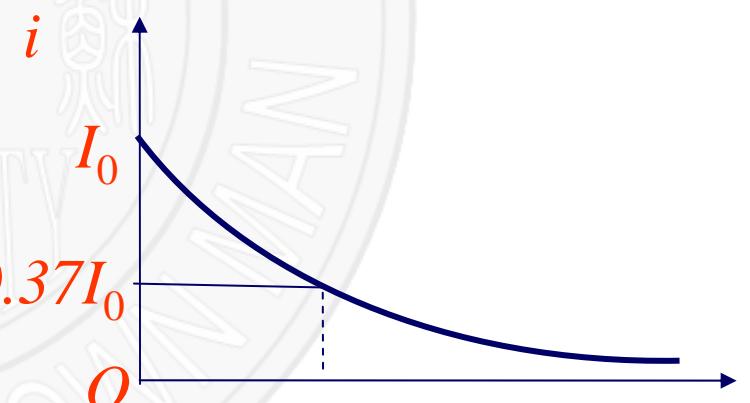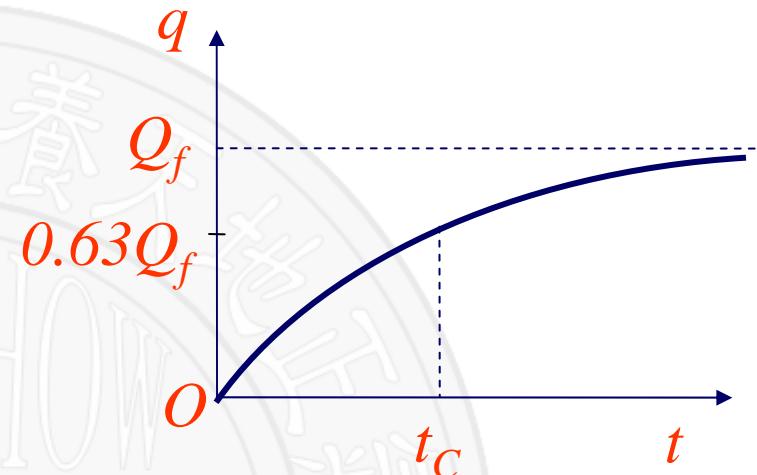
$$i = \frac{dq}{dt} = \frac{\varepsilon}{R} e^{-\frac{t}{RC}} = I_0 e^{-\frac{t}{RC}}$$



5.4 Transient Process

◆ The R-C Circuit

▲ time constant

$$\tau = RC \quad RC : \text{time unit}$$


* Switch Down: Discharging

According to Kirchhoff's
Second Law, we get

$$iR + \frac{q}{C} = 0$$


$$i = \frac{dq}{dt} \quad \frac{d q}{d t} = - \frac{q}{RC}$$

differential equation

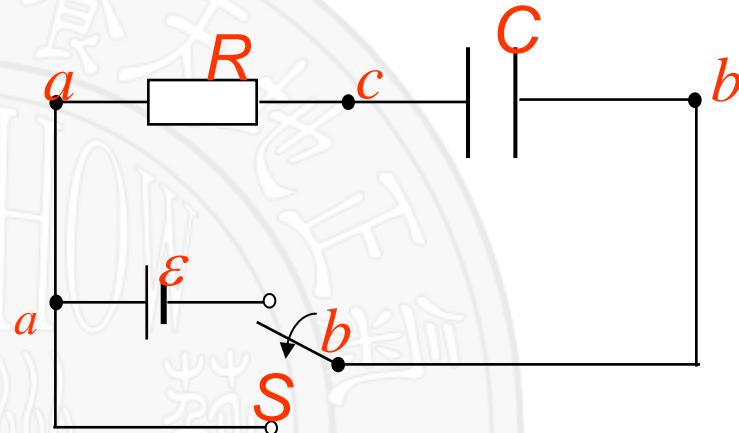

Show Capacitor
Charging & Discharging

From www.Youtube.com

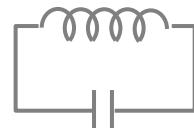

5.4 Transient Process

◆ The R-C Circuit


* Switch Down: Discharging

$$\int_{Q_f}^q \frac{dq}{q} = - \int_0^t \frac{dt}{RC}$$

$$\ln\left(\frac{q}{Q_f}\right) = -\frac{t}{RC}$$

$$q = Q_f e^{-\frac{t}{RC}}$$
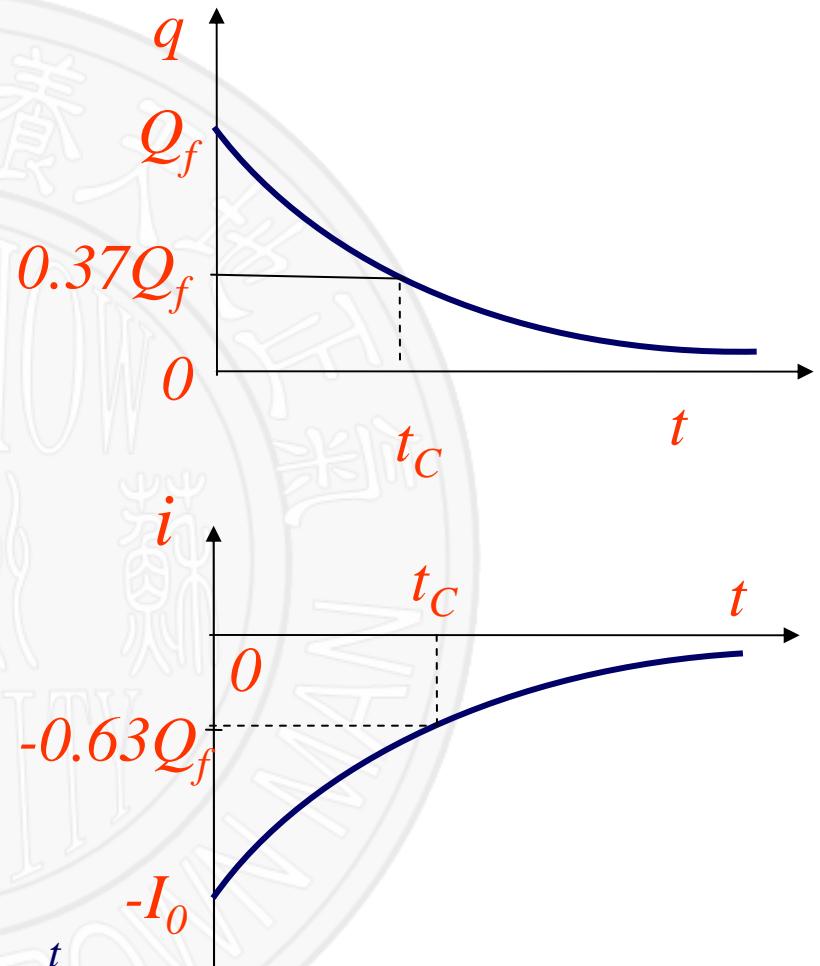
$$i = \frac{dq}{dt} = -\frac{Q_f}{RC} e^{-\frac{t}{RC}} = -I_0 e^{-\frac{t}{RC}}$$



5.4 Transient Process

◆ The L-C Circuit


* Switch up

From Kirchhoff's Second Law,
we get

$$\frac{q}{C} + L \frac{di}{dt} - \varepsilon = 0$$

$$\frac{di}{dt} = \frac{d^2 q}{dt^2}$$

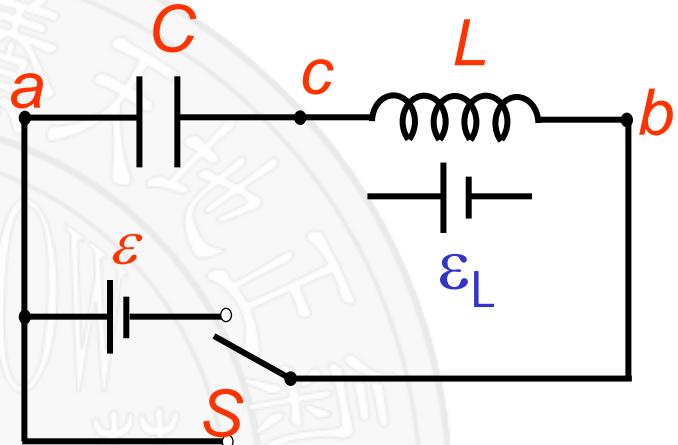
$$L \frac{d^2 q}{dt^2} + \frac{q}{C} - \varepsilon = 0$$



L-C Oscillation Circuit



Show RLC-Circuit

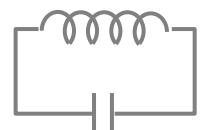

5.4 Transient Process

◆ The L-C Circuit

$$L \frac{d^2 q}{dt^2} + \frac{q}{C} - \varepsilon = 0$$



▲ General solution:

$$Q = C\varepsilon \cos\left(\frac{1}{\sqrt{LC}}t + \phi\right)$$

▲ Special solution:

$$\bar{q} = C\varepsilon$$
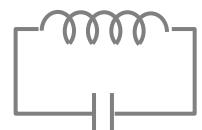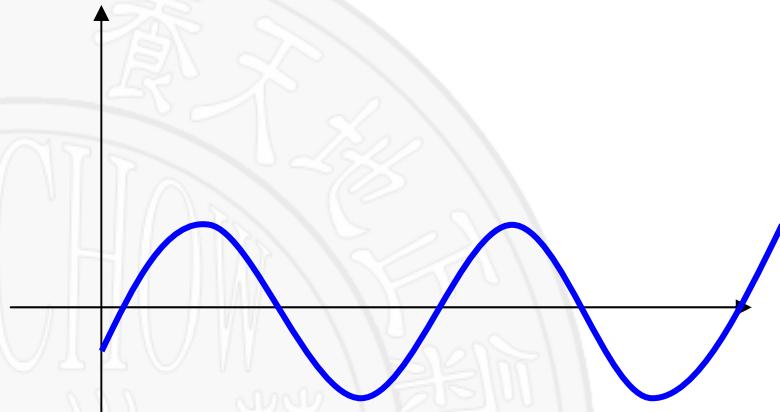
$$q = C\varepsilon \cos\left(\frac{1}{\sqrt{LC}}t + \phi\right) + C\varepsilon$$



5.4 Transient Process

◆ The L-C Circuit

* Switch Down

From Kirchhoff's Second Law,
we get




$$\frac{q}{C} + L \frac{di}{dt} = 0$$

$$L \frac{d^2 q}{dt^2} + \frac{q}{C} = 0$$

$$q = C\varepsilon \cos\left(\frac{1}{\sqrt{LC}}t + \phi\right)$$


$$\phi=0$$
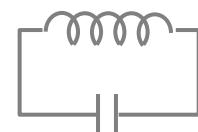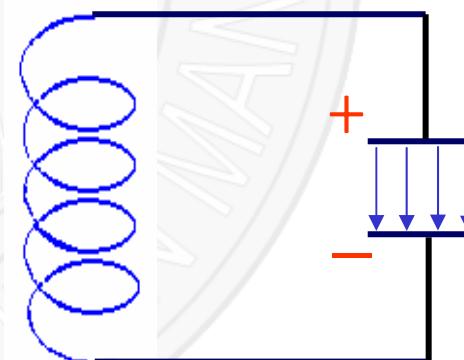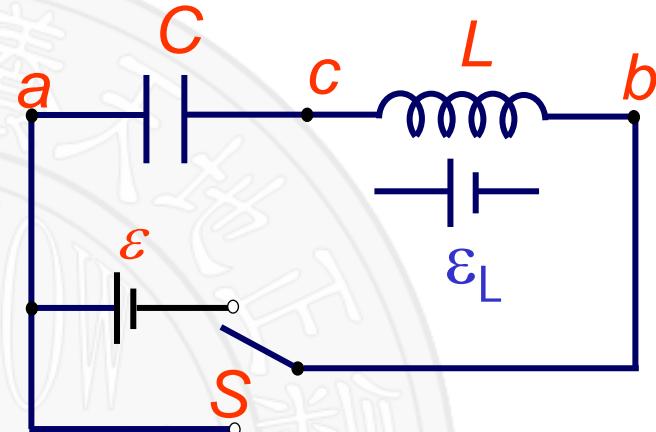
$$i = \frac{dq}{dt} = -\varepsilon \sqrt{\frac{C}{L}} \sin\left(\frac{1}{\sqrt{LC}}t\right)$$



5.4 Transient Process

The L-C Circuit

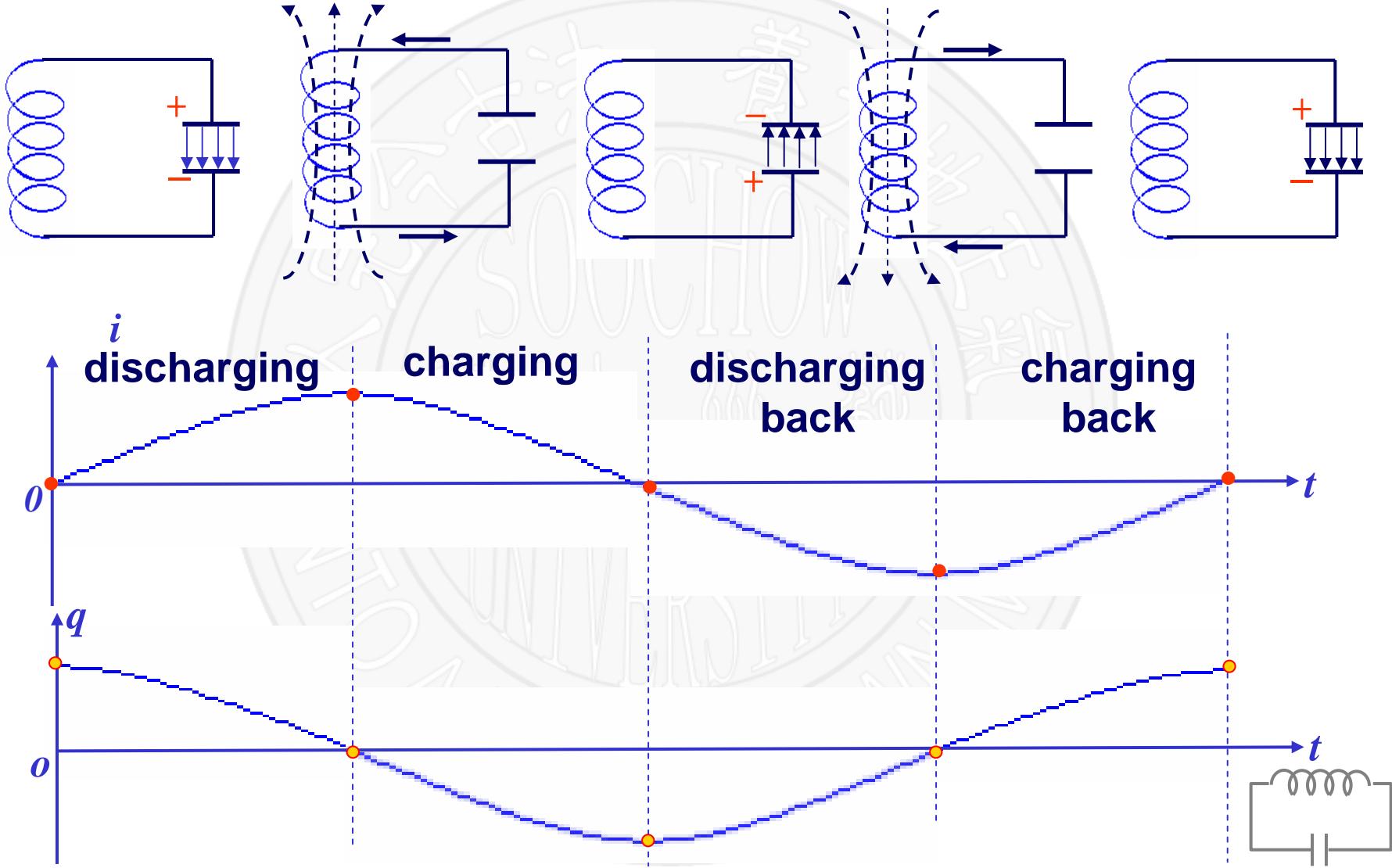

5.4 Transient Process

◆ The R-L-C Circuit


* Switch up

From Kirchhoff's Second Law,
we get

$$L \frac{di}{dt} + iR + \frac{q}{C} - \varepsilon = 0$$

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = \varepsilon$$

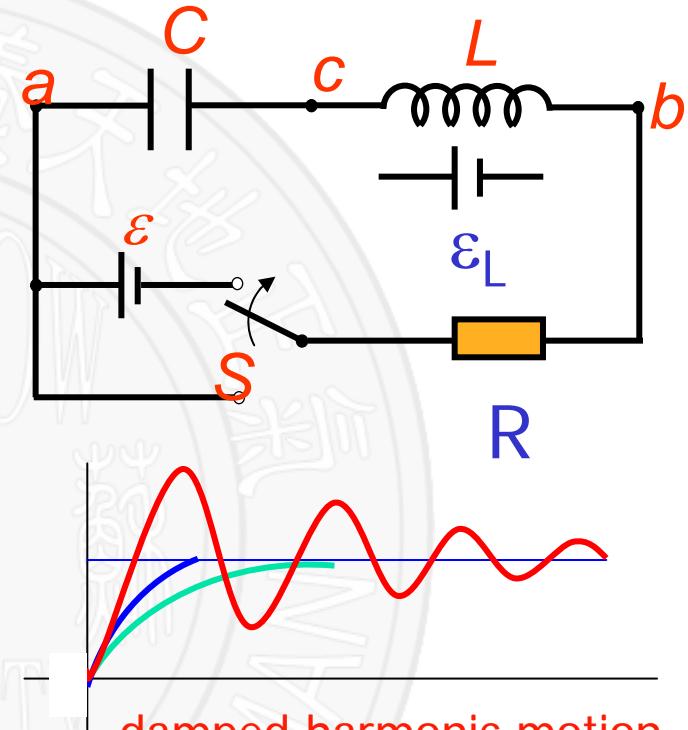resistance is to dissipate
the electromagnetic energy




damped harmonic motion

Overdamped

Critical damped

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$
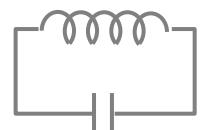
$$\nu = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$



5.4 Transient Process

◆ The R-L-C Circuit


* Switch down

From Kirchhoff's Second Law,
we get

$$L \frac{di}{dt} + iR + \frac{q}{C} = 0$$


$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$
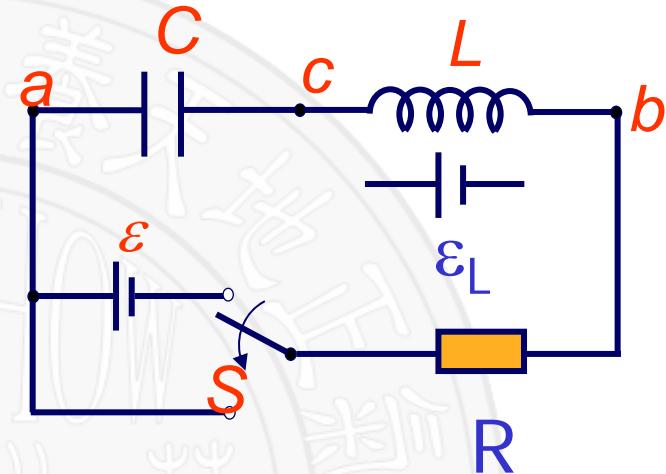
$$\omega_0^2 = \frac{1}{LC} \quad \beta = \frac{R}{2L}$$



$$\frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{q}{LC} = 0$$
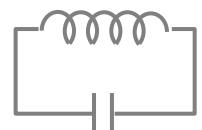
$$\frac{d^2q}{dt^2} + 2\beta \frac{dq}{dt} + \omega_0^2 q = 0$$



5.4 Transient Process

◆ The R-L-C Circuit

★ Switch down

If $\beta < \omega_0$




$$\beta = \frac{R}{2L}$$

$$\frac{R}{2L} < \sqrt{\frac{1}{LC}}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$q = \varepsilon C e^{-(R/2L)t} \cos\left(\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} t + \phi\right)$$

underdamped or damped
harmonic motion

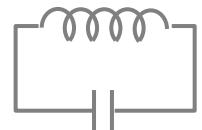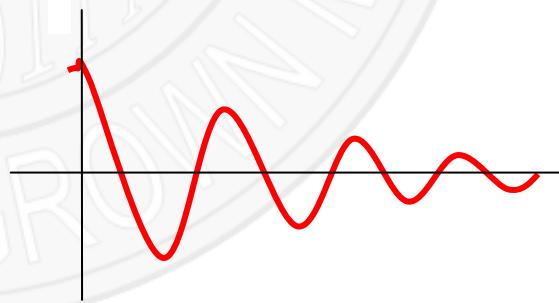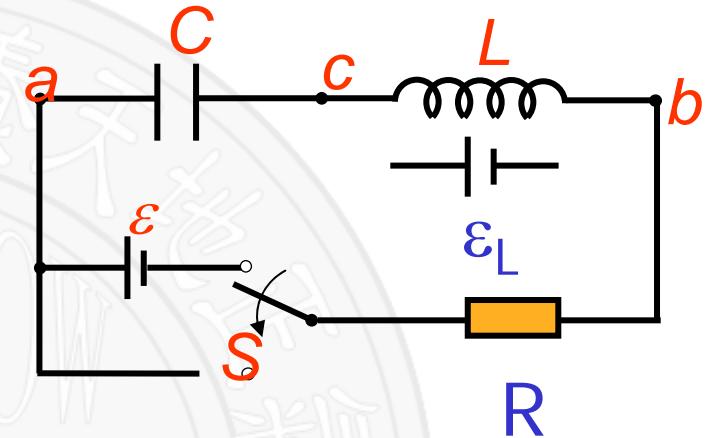

5.4 Transient Process

◆ The R-L-C Circuit

* *Critical damped motion*

If $\frac{R}{2L} = \sqrt{\frac{1}{LC}}$



Critical damped motion

$$q = (c\varepsilon + c't) e^{-\frac{R}{2L}t}$$

* *Over damped motion*

If $\frac{R}{2L} > \sqrt{\frac{1}{LC}}$
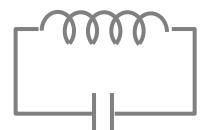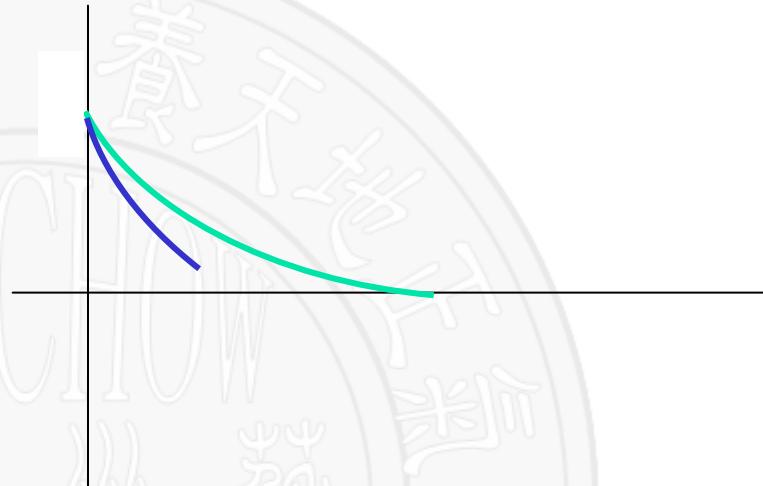
$$q = \frac{1}{2} C\varepsilon (e^{-[\frac{R}{2L} - \sqrt{(\frac{R}{2L})^2 - (\frac{1}{LC})}]t} + e^{-[\frac{R}{2L} + \sqrt{(\frac{R}{2L})^2 - (\frac{1}{LC})}]t})$$



5.4 Transient Process

◆ The R-L-C Circuit

Example 5.9 A resistor of resistance $R = 10 \text{ M}\Omega$ is connected in series with a capacitor of capacitance $1\mu\text{F}$. Find the time constant τ .

Solution:

From formula of the time constant, we get

$$\tau = RC = (10 \times 10^6 \times 10^{-6}) = 10 \text{ (s)},$$

the half-life is

$$t_h = (10 \ln 2) = 6.9 \text{ (s)}.$$

On the other hand, if $R = 10\Omega$, the time constant is only $10 \times 10^{-6} \text{ s}$, or $10 \mu\text{s}$.

