

补例4 已知：电感无初始储能 $t = 0$ 时合 S_1 , $t = 0.2s$ 时合 S_2 , 求两次换路后的电感电流 $i(t)$ 。


解 $0 < t < 0.2s$

$$i(0_+) = i(0_-) = 0$$

$$t_1 = L/R = 1/5 = 0.2s$$

$$i(\infty) = 5/5 = 1A$$

$$i(t) = 1 - e^{-5t} \text{ A}$$

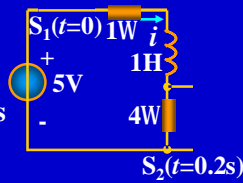


$$t > 0.2s \quad i(0.2_+) = 1 - e^{-5 \cdot 0.2} = 0.63$$

$$i(0.2_+) = 0.63A$$

$$t_2 = L/R = 1/1 = 1$$

$$i(\infty) = 5/1 = 5A$$

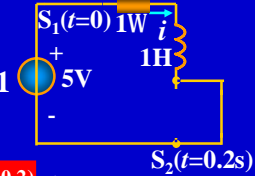
$$i(t) = 5 - 4.37e^{-(t-0.2)} \text{ A}$$



注意

$$i = 1 - e^{-5t} \quad (0 < t \leq 0.2s)$$
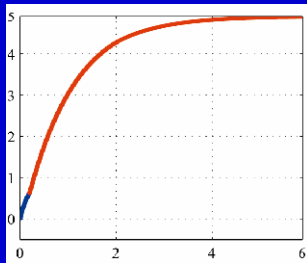
$$i = 5 - 4.37e^{-(t-0.2)} \quad (t \geq 0.2s)$$




§ 7-7 一阶电路的阶跃响应

一、单位阶跃函数 $e(t)$

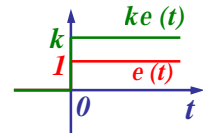
1、定义

$$e(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$



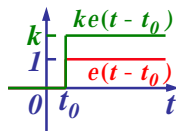
2、延迟的单位阶跃函数

$$e(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$









3、单位阶跃函数的作用


• 模拟开关

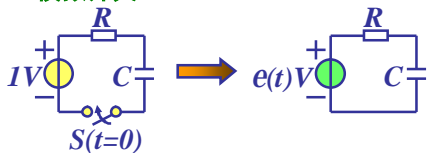


```
clear; t=-1:0.01:3; f1=t; f2=t.*stepfun(t,0);
f3=t.*stepfun(t-1,0); f4=(t-1).*stepfun(t-1,0);
subplot 221; plot(t,f1,'k','LineWidth',3);
axis([-1 3 -1 3]);grid on
subplot 222; plot(t,f1,'k','LineWidth',3);
hold on; plot(t,f2,'b','LineWidth',3);
axis([-1 3 -1 3]);grid on
subplot 223; plot(t,f1,'k','LineWidth',3);
hold on; plot(t,f3,'g','LineWidth',3);
axis([-1 3 -1 3]);grid on
subplot 224; plot(t,f2,'b','LineWidth',3);
hold on; plot(t,f4,'r','LineWidth',3);
axis([-1 3 -1 3]);grid on
```

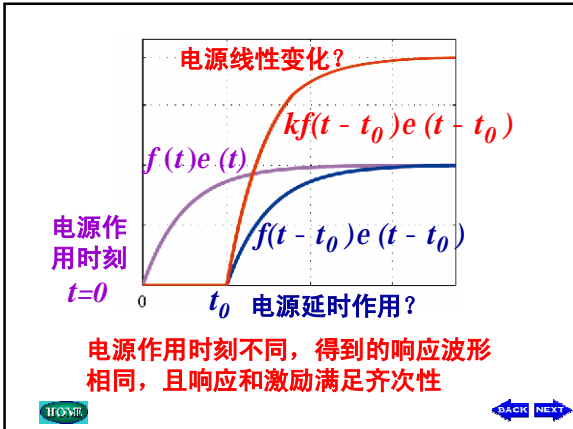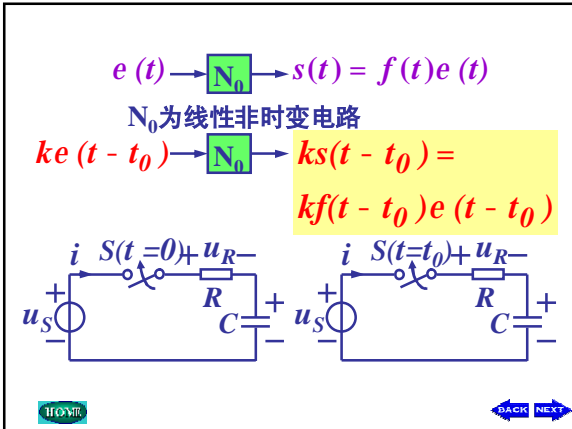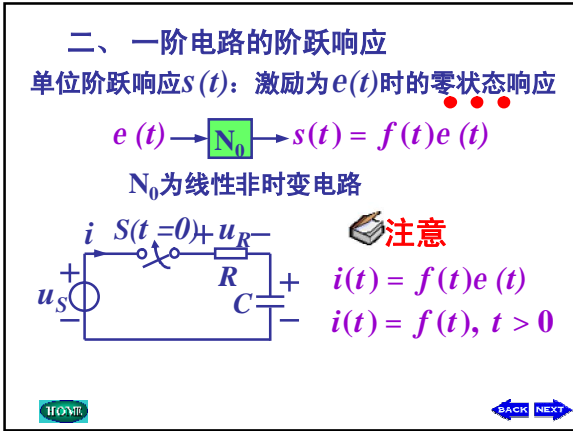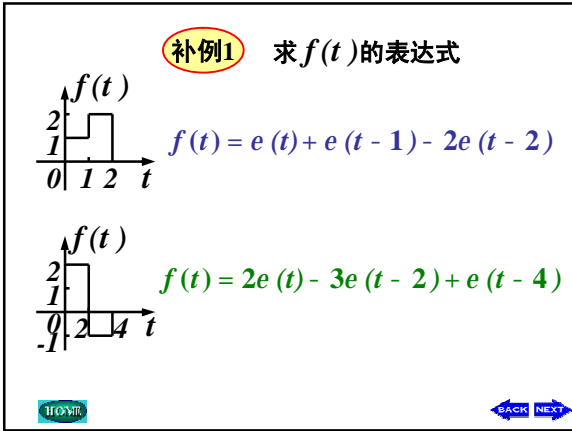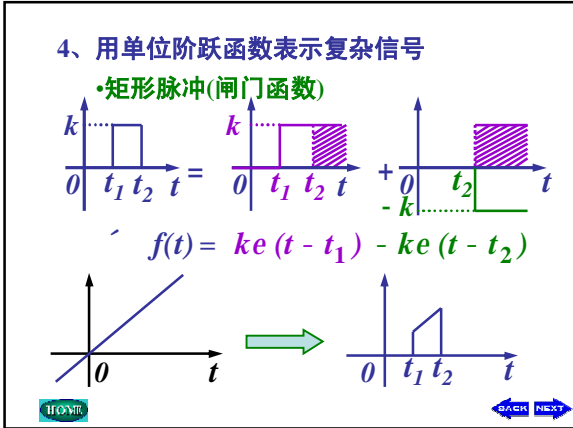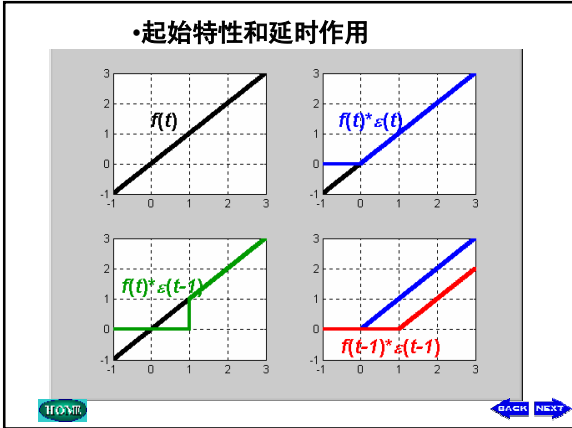

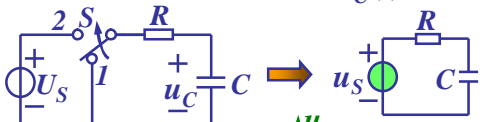例7-11 电路原已达稳态，在 $t = 0$ 时开关由位置1合向位置2，在 $t = t$ 时又由位置2合向位置1，求 $t \geq 0$ 时的 $u_C(t)$



解：电路可等效为

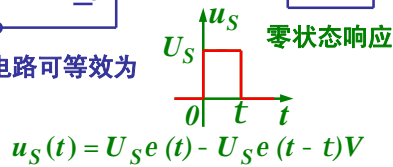

1、先求单位阶跃响应

$$u_C = u_C(\infty)(1 - e^{-\frac{t}{RC}})V$$

$$u_S = e(t) \quad \text{且} \quad s(t) = (1 - e^{-\frac{t}{\tau}})e(t)V$$

2、根据线性时不变关系写出零状态响应

$$u_S(t) = U_S e(t) - U_S e(t-t)V$$

$$u_C(t) = \underbrace{U_S(1 - e^{-\frac{t}{\tau}})e(t)}_{\downarrow \frac{t}{\tau}} - \underbrace{U_S(1 - e^{-\frac{t-t}{\tau}})e(t-t)}_{\downarrow \frac{t-t}{\tau}}V$$

•分段表示为：

$$u_C(t) = U_S(1 - e^{-\frac{t}{\tau}})e(t) - U_S(1 - e^{-\frac{t-t}{\tau}})e(t-t)V$$

$$0 < t < \tau \quad u_C(t) = U_S(1 - e^{-\frac{t}{\tau}})V$$

$$\begin{aligned} t > \tau \\ u_C(t) &= U_S(1 - e^{-\frac{t}{\tau}}) - U_S(1 - e^{-\frac{t-t}{\tau}}) \\ &= U_S(e^{-\frac{t-t}{\tau}} - e^{-\frac{t}{\tau}}) = U_S e^{-\frac{t-t}{\tau}}(1 - e^{-1}) \\ &= 0.632U_S e^{-\frac{t-t}{\tau}}V \end{aligned}$$

•分段表示为：




$$u_C(t) = U_S(1 - e^{-\frac{t}{\tau}})e(t) - U_S(1 - e^{-\frac{t-t}{\tau}})e(t-t)V$$



$$0 < t < \tau \quad u_C(t) = U_S(1 - e^{-\frac{t}{\tau}})V$$

$$t > \tau \quad u_C(t) = 0.632U_S e^{-\frac{t-t}{\tau}}V$$

$$\begin{aligned} u_C(t) &= U_S(1 - e^{-\frac{t}{\tau}})[e(t) - e(t-t)] \\ &\quad - 0.632U_S e^{-\frac{t-t}{\tau}}e(t-t)V \end{aligned}$$
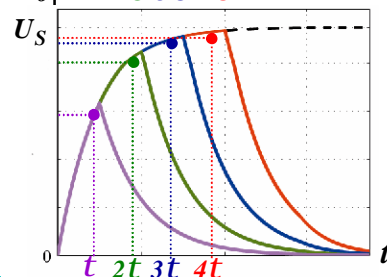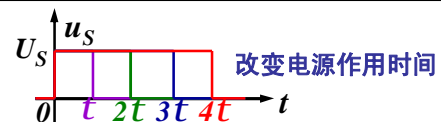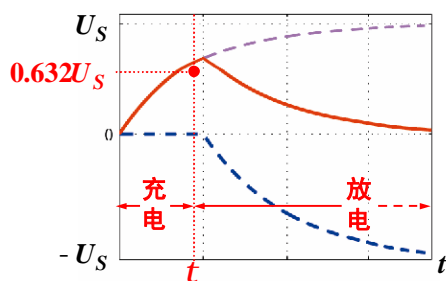
$$u_C(t) = U_S(1 - e^{-\frac{t}{\tau}})e(t) - U_S(1 - e^{-\frac{t-t}{\tau}})e(t-t)V$$



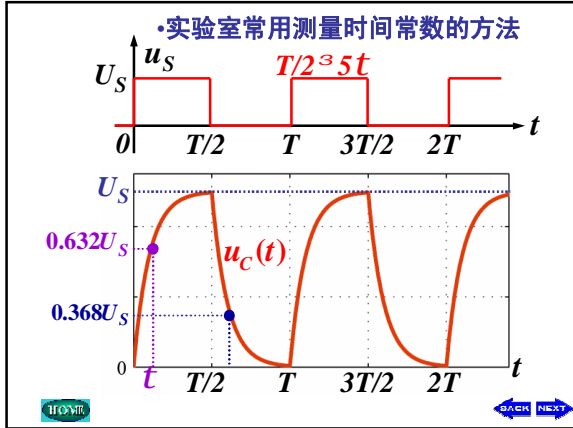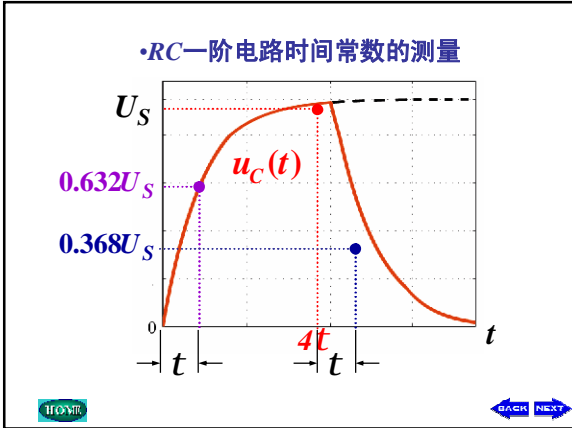

补例2 求: $t \geq 0$ 时的 $i_L(t)$


$S_1(t=0)$ $S_2(t=0)$

$4V$ $1W$ i_L $1W$ u i_S $L=1H$ $\frac{2}{1}$ 0 1 2 t

解: 全响应分为 零输入响应 + 零状态响应
 $i_L(t) = i_L'(t) + i_L''(t)$
 $i_L'(t) = 4e^{-2t} A$ 具体计算过程见7-4补例1

先求单位阶跃响应 能否由下式推出?

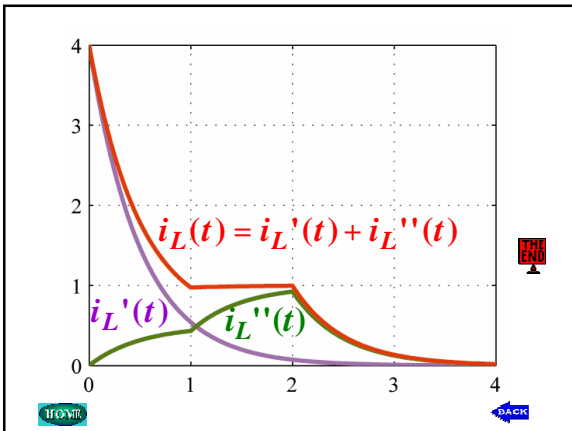$i_S = 2A$ 作用, 零状态响应 $i_L'' = 1 - e^{-2t} A$
 $i_S = e(t) \quad \text{D} \quad s(t) = (0.5 - 0.5e^{-2t}) e(t) A$
 根据线性非时变关系写出零状态响应
 $i_S(t) = e(t) + e(t-1) - 2e(t-2) A$ *
 $i_L''(t) = s(t) + s(t-1) - 2s(t-2)$
 $= (0.5 - 0.5e^{-2t})e(t) + (0.5 - 0.5e^{-2(t-1)})e(t-1)$
 $- 2 \times (0.5 - 0.5e^{-2(t-2)})e(t-2) A$



§ 7-8 一阶电路的冲激响应

一、单位冲激函数 $d(t)$ $d(t) = 0, t < 0$
 1、定义 $\int_{-\infty}^{\infty} d(t) dt = 1$

$\frac{1}{D}$ $\frac{1}{D}$ D t
 单位冲激函数

2、延迟的单位冲激函数

3、单位冲激函数的性质 $\frac{de(t)}{dt} = d(t)$;

$$\int_{-\infty}^{\infty} f(t) \times d(t) dt = \int_{0^-}^{0^+} f(0) \times d(t) dt = f(0)$$

$$f(t) \times d(t - t_0) = f(t_0) \times d(t - t_0)$$

$$\int_{-\infty}^{\infty} f(t) \times d(t - t_0) dt = f(t_0) \quad \text{积分=?}$$

Navigation: BACK NEXT

二、一阶电路的冲激响应

单位冲激响应 $h(t)$: 激励为 $d(t)$ 时的零状态响应

补例 $i_L(0_-) = 0$, 求: $t \geq 0$ 时的 $i_L(t), u_L(t)$

$$i = u = i_L + u_L$$

$$= i_L + L \frac{di_L}{dt}$$

$$\begin{cases} \frac{di_L}{dt} + 2i_L = d(t) \\ i_L(0_-) = 0 \end{cases}$$

解: $i + i_L = d(t)$

Navigation: BACK NEXT

$$\begin{cases} \frac{di_L}{dt} + 2i_L = d(t) & i_L = kd(t) \\ i_L(0_-) = 0 & i = (1-k)d(t) \\ & u = i^{-1} kd(t) + d'(t) \end{cases}$$

积分=0

$$\int_{0^-}^{0^+} \frac{di_L}{dt} dt + \int_{0^-}^{0^+} 2i_L dt = \int_{0^-}^{0^+} d(t) dt$$

$$\int_{0^-}^{0^+} di_L = 1$$

$$\int_{0^-}^{0^+} \frac{di_L}{dt} + 2i_L dt = 0$$

$$i_L(0_+) = 1$$

Navigation: BACK NEXT

$$\begin{cases} \frac{di_L}{dt} + 2i_L = 0 \\ i_L(0_+) = 1 \end{cases} \quad \text{零输入响应}$$

$$i_L(t) = e^{-\frac{t}{L}} e(t) = e^{-2t} e(t) A$$

$$u_L(t) = L \frac{di_L}{dt} = -2e^{-2t} e(t) + e^{-2t} d(t)$$

$$= -2e^{-2t} e(t) + d(t) V$$

Navigation: BACK NEXT

•实际计算时可采用下面的方法:

- $0_- \text{ @ } 0_+$ 时刻, $d(t)$ 作用, $u_C(0_+)$ 、 $i_L(0_+)$ 变化

$$\int_{0^-}^{0^+} \dot{u}_C(0_+) = u_C(0_-) + \frac{1}{C} \int_{0^-}^{0^+} i_C(t) dt$$

$$\int_{0^-}^{0^+} \dot{i}_L(0_+) = i_L(0_-) + \frac{1}{L} \int_{0^-}^{0^+} u_L(t) dt$$

- $t > 0_+$, $d(t) = 0$

$u_C(0_+)$ 、 $i_L(0_+)$ 引起零输入响应

Navigation: BACK NEXT

补例 $i_L(0_-) = 0$, 求: $t \geq 0$ 时的 $i_L(t), u_L(t)$

解: 1、求 $u_L(0)$

$$u_L(0) = d(t) V$$

$$i_L(0_+) = i_L(0_-) + \frac{1}{L} \int_{0^-}^{0^+} u_L(0) dt$$

$$= 0 + \int_{0^-}^{0^+} d(t) dt = 1 A$$

Navigation: BACK NEXT

$t \geq 0_+$ 时:

$$i_L(t) = e^{-\frac{t}{\tau}} e(t) = e^{-2t} e(t) A$$

$$u_L(t) = -2e^{-2t} e(t) + d(t) V$$

单位阶跃响应见7-7补例2

$$\frac{ds(t)}{dt} = \frac{d[(0.5 - 0.5e^{-2t})e(t)]}{dt}$$

$$= e^{-2t} e(t) A = h(t)$$

单位冲激响应和单位阶跃响应的关系

