

## § 9-4 正弦稳态电路的功率

### 一、瞬时功率 $p$


(instantaneous power)

$$u = \sqrt{2}U \cos(\omega t + y_u) \text{ V}$$

$$i = \sqrt{2}I \cos(\omega t + y_i) \text{ A} \quad j = y_u - y_i$$

$$p = ui$$
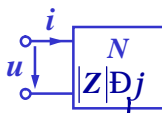
$$= UI \cos(y_u - y_i) + UI \cos(2\omega t + y_u + y_i)$$




HOME

BACK NEXT

$$p = UI \cos j + UI \cos(2\omega t + y_u + y_i)$$
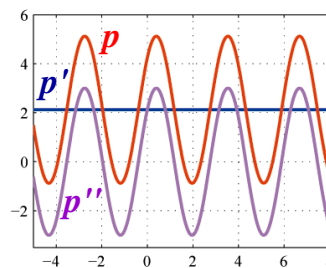
$$= p' + p'' = \text{恒定分量} + \text{正弦分量}$$



HOME


BACK NEXT

$$p = UI \cos j \{1 + \cos[2(\omega t + y_u)]\}$$

$$+ UI \sin j \cos[2(\omega t + y_u)]$$

不可逆部分  
可逆部分

$$= p' + p''$$

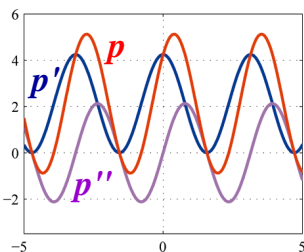

HOME

BACK NEXT

### 二、平均(有功)功率 $P = UI \cos j$

(average power)

功率因数

$$P = \frac{1}{T} \int_0^T p dt$$

感性电路: 滞后  
容性电路: 超前

$$= \frac{1}{T} \int_0^T \{UI \cos j + UI \cos(2\omega t + y_u + y_i)\} dt$$

$$P_R = UI \cos 0^\circ = UI$$

$$R, L, C \text{ 的 } P: P_L = UI \cos 90^\circ = 0$$

$$P_C = UI \cos(-90^\circ) = 0$$

$P$  为消耗在网络中各电阻上的功率之和

$$P = UI \cos j = \dot{a} P_{Rk}$$

HOME

BACK NEXT

### 三、无功功率 $Q = UI \sin j$

(reactive power)

单位: var

$$R, L, C \text{ 的 } Q: Q_R = UI \sin 0^\circ = 0$$

$$Q_L = U_L I_L \sin 90^\circ = U_L I_L = I_L^2 X_L = \frac{U_L^2}{X_L}$$

$$Q_C = U_C I_C \sin(-90^\circ) = -U_C I_C = I_C^2 X_C = \frac{U_C^2}{X_C}$$

感性电路:

容性电路:

$$0 < j < 90^\circ, Q > 0 \quad -90^\circ < j < 0, Q < 0$$

$$Q = \dot{a} Q_{Lk} + \dot{a} Q_{Cj}$$

HOME

BACK NEXT


### 四、视在功率 $S = UI$

(apparent power)

功率三角形

$$P = S \cos j$$

$$Q = S \sin j$$

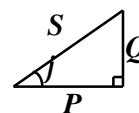

$$S = \sqrt{P^2 + Q^2}$$

功率因数:

$$j = \text{tg}^{-1} \frac{Q}{P} \quad PF = \cos j = \frac{P}{S}$$

HOME

BACK NEXT

$Z = R + j(X_L + X_C) = R + jX = |Z| \angle \phi$   
 $U_S = ZI = U_R + U_X$   
 $U_S = |Z|I$   
 $U_R = RI, U_X = |X|I$   
 $P = RI^2 = U_R I$  阻抗  $\frac{I}{I}$  电压  $\frac{I}{I}$  功率  $\frac{I}{I}$   
 $Q = |X|I^2 = U_X I$  电阻  $\frac{I}{I}$  电压  $\frac{I}{I}$  功率  $\frac{I}{I}$   
 $U_R$  有功分量  $U_X$  无功分量


无功功率有正负???  
 电感、电容的无功补偿作用

$Y = G + j(B_L + B_C) = G + jB = |Y| \angle -\phi$   
 $I_S = YU = I_G + I_B$   
 $I_S = |Y|U$   
 $I_G = GU, I_B = |B|U$   
 $P = GU^2 = I_G U$  导纳  $\frac{U}{U}$  电流  $\frac{U}{U}$  功率  $\frac{U}{U}$   
 $Q = BU^2 = I_B U$  电阻  $\frac{U}{U}$  电压  $\frac{U}{U}$  功率  $\frac{U}{U}$   
 $I_G$  有功分量  $I_B$  无功分量

**补例1** 三表法测线圈参数。  
 已知:  $f=50\text{Hz}$ , 且测得  $U=50\text{V}$ ,  $I=1\text{A}$ ,  $P=30\text{W}$ 。  
**解法 1**  
 $S = UI = 50\text{VA}$   
 $Q = \sqrt{S^2 - P^2} = 40\text{var}$   
 $R = \frac{P}{I^2} = \frac{30}{1} = 30\Omega$   $X_L = \frac{Q}{I^2} = \frac{40}{1} = 40\Omega$   
 $L = \frac{X_L}{\omega} = \frac{40}{100\pi} = 0.127\text{H}$

已知:  $f=50\text{Hz}$ , 且  $U=50\text{V}$ ,  $I=1\text{A}$ ,  $P=30\text{W}$ 。  
**解法 2**  
 $P = UI \cos \phi$   
 $\cos \phi = \frac{P}{UI} = 0.6$   
 $|Z| = \frac{U}{I} = 50\Omega$   $R = |Z| \cos \phi = 30\Omega$   
 $X_L = |Z| \sin \phi = 40\Omega$

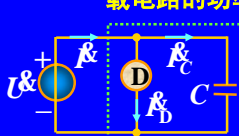**补例2** 已知: 电动机  $P_D=1000\text{W}$ ,  $U=220\text{V}$ ,  $f=50\text{Hz}$ ,  $C=30\text{mF}$ ,  $\cos\varphi_D=0.8$ , 求: 负载电路的功率因数。



**解**  $I_D = \frac{P_D}{U \cos\varphi_D} = 5.68\text{A}$

$\cos\varphi_D = 0.8$  (感性),  $\varphi_D = 36.8^\circ$

设  $\dot{U} = 220\angle 0^\circ \text{V}$

$\dot{I}_D = 5.68\angle -36.8^\circ \text{A}$

$\dot{I}_C = 220\angle 0^\circ \times j\omega C = j2.08\text{A}$

$\dot{I} = \dot{I}_D + \dot{I}_C = 4.73\angle -16.3^\circ \text{A}$

$\cos\varphi = \cos[0^\circ - (-16.3^\circ)] = 0.96$

HOME BACK

### § 9-5 复功率(Complex Power)

$$\tilde{S} \stackrel{\text{def}}{=} \dot{U} \dot{I}^* = \dot{Z} \dot{I} \dot{I}^* = \dot{Z} I^2 = \dot{Y}^* U^2$$

$$\tilde{S} = \dot{U} \dot{Y}_u \times \dot{I} \dot{Y}_i = \dot{U} \dot{Y}_u - \dot{Y}_i$$


不是相量  $= S \angle j = P + jQ$

$$P = \dot{a} P_k \quad \tilde{S} = \dot{a} \tilde{S}_k$$

$$Q = \dot{a} Q_k \quad S^{-1} \dot{a} S_k$$

HOME NEXT

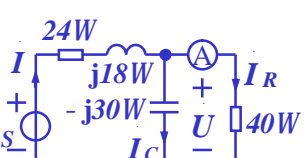**补例1** 电流表读数为1.5A, 求电源供出的  $\tilde{S}, S, P, Q$




**解:**  $U = 1.5 \times 40 = 60\text{V}$

令:  $\dot{U} = 60\angle 0^\circ \text{V} \quad \dot{I}_R = 1.5\angle 0^\circ \text{A}$

$$\dot{I}_C = \frac{60\angle 0^\circ}{-j30} = 2\angle 90^\circ \text{A}$$

HOME BACK NEXT

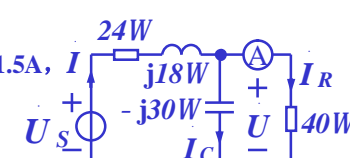**补例1** 电流表读数为1.5A, 求电源供出的  $\tilde{S}, S, P, Q$




$$\dot{I} = \dot{I}_R + \dot{I}_C = 1.5 + j2 = 2.5\angle 53.13^\circ \text{A}$$

$$\dot{U}_S = (24 + j18) \times \dot{I} + \dot{U}$$

$$= 60 + j75 = 96.05\angle 51.34^\circ \text{V}$$

HOME BACK NEXT

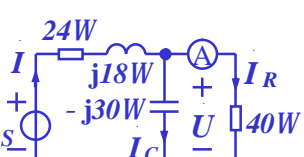**补例1** 电流表读数为1.5A, 求电源供出的  $\tilde{S}, S, P, Q$



$$\tilde{S} = \dot{U}_S \dot{I}^* = 96.05\angle 51.34^\circ \times 2.5\angle -53.13^\circ$$

$$= 240.13\angle -1.79^\circ = 240 - j7.5$$

$P = 240\text{W}, Q = -7.5 \text{ var}, S = 240.13\text{VA}$

HOME BACK NEXT

**补例2** 功率因数的提高

$$P = UI \cos\varphi = S \cos\varphi$$

75kVA 负载  $\cos\varphi = 1, P=S=75\text{kW}$   
 $\cos\varphi = 0.7, P=0.7S=52.5\text{kW}$

一般用户: 异步电机 空载  $\cos\varphi = 0.2\sim 0.3$   
 满载  $\cos\varphi = 0.7\sim 0.85$   
 日光灯  $\cos\varphi = 0.45\sim 0.6$

1、S一定,  $\cos\varphi \uparrow, P \uparrow$   
 2、P, U一定,  $\cos\varphi \uparrow, I \downarrow$

HOME BACK NEXT

功率因数的提高  $P = UI \cos j = S \cos j$

$j_2 < j_1, \cos j_2 > \cos j_1$

$Q_1 = P \operatorname{tg} j_1, Q_2 = P \operatorname{tg} j_2$

$Q_C = Q_2 - Q_1$

$= P \operatorname{tg} j_2 - P \operatorname{tg} j_1$

$= U^2 / X_C = -w C U^2$

$C = \frac{P \operatorname{tg} j_1 - P \operatorname{tg} j_2}{w U^2}$

欠/过补偿

HOME BACK NEXT

欠/过补偿

有功分量

无功分量

补偿电流的无功分量  $I_2 \cos j_2 = I_1 \cos j_1$

$I_1 = \frac{P}{U \cos j_1}$

$I_2 = \frac{I_1 \cos j_1}{\cos j_2}$

$I_C = I_1 \sin j_1 - I_2 \sin j_2 = \frac{U}{|X_C|} = w C U$

HOME BACK NEXT

§ 9-6 最大功率传输  
(Maximum Average Power Transfer)

$I = \frac{U_{oc}}{Z_{eq} + Z}$

$= \frac{U_{oc}}{(R_{eq} + R) + j(X_{eq} + X)}$

$P = I^2 R = \frac{U_{oc}^2 R}{\sqrt{(R_{eq} + R)^2 + (X_{eq} + X)^2}^2}$

HOME BACK NEXT

$P = \frac{U_{oc}^2 R}{(R_{eq} + R)^2 + (X_{eq} + X)^2}$

若R, X都可变  $P = \frac{U_{oc}^2}{(R_{eq} + R)^2} R$  \*

$X_{eq} + X = 0, R = R_{eq}$

即  $Z = R_{eq} - jX_{eq} = Z_{eq}^*$   $P_{max} = \frac{U_{oc}^2}{4R_{eq}}$

最佳匹配

HOME BACK NEXT

若为诺顿等效电路, 则当  $Y = Y_{eq}^*$

$P_{max} = \frac{I_{sc}^2}{4G_{eq}}$

若Z=R为纯电阻

获得最大功率条件: 模匹配

$R = \sqrt{R_{eq}^2 + X_{eq}^2} = |Z_{eq}|$

HOME BACK NEXT

补例1 求最佳匹配时获得的最大功率

$I_S = 2 \angle 0^\circ A$

$2W$   $2W$   $2W$   $j4W$   $U$   $I$   $Z$

HOME BACK NEXT

**补例1** 求最佳匹配时获得的最大功率

解:

$$U_{oc} = \frac{2 \times 2 \angle 0^\circ}{2 + 2 + j4} \times j4 = 2\sqrt{2} \angle 45^\circ \text{V}$$

HOME BACK NEXT

**补例1** 求最佳匹配时获得的最大功率

解:

$$U_{oc} = \frac{2 \times 2 \angle 0^\circ}{2 + 2 + j4} \times j4 = 2\sqrt{2} \angle 45^\circ \text{V}$$

$$Z_{eq} = (2 + 2) // j4 = 2 + j2 \Omega$$

HOME BACK NEXT

**补例1** 求最佳匹配时获得的最大功率

当  $Z = Z_{eq}^* = 2 - j2 \Omega$  时

$$P_{max} = \frac{U_{oc}^2}{4R_{eq}} = 1 \text{W}$$

HOME BACK NEXT

**补例2** 电路如图, 求:  $1. R_L = 5 \Omega$  时其消耗的功率;

解:

$$Z_{eq} = R + jX_L = 5 + j10^5 \cdot 50 \cdot 10^{-6} = 5 + j5 \text{ W}$$

$$I = \frac{10 \angle 0^\circ}{5 + j5 + 5} = 0.89 \angle (-26.6^\circ) \text{ A}$$

$$P_L = I^2 R_L = 0.89^2 \cdot 5 = 4 \text{ W}$$

HOME BACK NEXT

2.  $R_L = ?$  能获得最大功率, 并求最大功率;

$$Z_{eq} = 5 + j5 \text{ W}$$

当  $R_L = \sqrt{R_{eq}^2 + X_{eq}^2} = \sqrt{5^2 + 5^2} = 7.07 \text{ W}$  获最大功率

$$I = \frac{10 \angle 0^\circ}{5 + j5 + 7.07} = 0.766 \angle (-22.5^\circ) \text{ A}$$

$$P_L = I^2 R_L = 0.766^2 \cdot 7.07 = 4.15 \text{ W}$$

HOME BACK NEXT

3. 在  $R_L$  两端并联一电容, 问  $R_L$  和  $C$  为多大时能与内阻抗最佳匹配, 并求最大功率。

$$Z_{eq} = 5 + j5 \text{ W}$$

$$Z_L = \frac{1}{Y} = \frac{R_L}{1 + j\omega C R_L} = \frac{R_L}{1 + (j\omega C R_L)^2} = \frac{R_L}{1 - (\omega C R_L)^2} - j \frac{\omega C R_L^2}{1 - (\omega C R_L)^2}$$

令  $R_L = 10 \text{ W}$  获最大功率  $P_{max} = \frac{U_{oc}^2}{4R_{eq}} = 5 \text{ W}$

令  $C = 1 \text{ mF}$

HOME BACK NEXT