

§ 8-4 电路定律的相量形式

一、KCL、KVL的相量形式

$$\begin{aligned} \dot{a}i &= 0 & \dot{a}I &= 0 \\ \dot{a}u &= 0 & \dot{a}U &= 0 \end{aligned} \quad \text{P}$$

HOME

NEXT

二、VCR的相量形式


$$U = U \mathcal{D} y_u \quad I = I \mathcal{D} y_i$$

1、R



$$u = Ri \quad \text{P} \quad \dot{U} = R \dot{I}$$


向量图
相量图

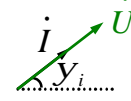

$$\begin{aligned} \dot{U} &= RI \\ \dot{Y}_u &= y_i \end{aligned}$$

HOME


BACK NEXT

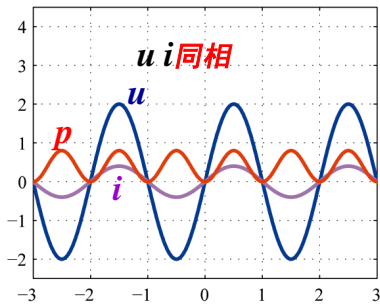


HOME

BACK NEXT

2、L

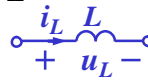
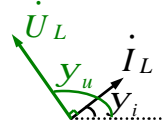
$$u_L = L \frac{di_L}{dt} \quad U_L = j\omega L I_L \quad \text{感纳}$$




$$\begin{aligned} U_L &= jX_L I_L, \quad I_L = jB_L U_L \\ \dot{U}_L &= \omega L \dot{I}_L = X_L \dot{I}_L \\ \dot{Y}_u &= y_i + 90^\circ \end{aligned}$$

HOME

BACK NEXT



u超前于i 正交

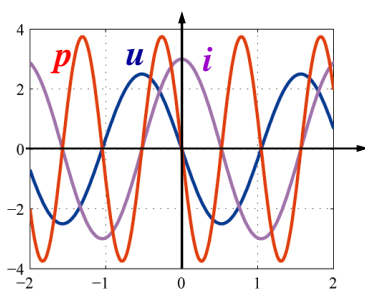


HOME

BACK NEXT

3、C

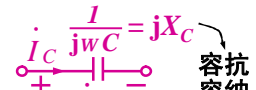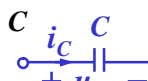

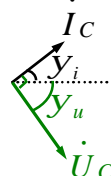
$$i_c = C \frac{du_c}{dt} \quad I_c = j\omega C U_c = jB_C U_c$$



$$\begin{aligned} U_c &= \frac{1}{j\omega C} I_c = jX_C I_c \\ \dot{U}_c &= \frac{1}{\omega C} \dot{I}_c = |X_C| \dot{I}_c \\ \dot{Y}_u &= y_i - 90^\circ \end{aligned}$$

HOME

BACK NEXT

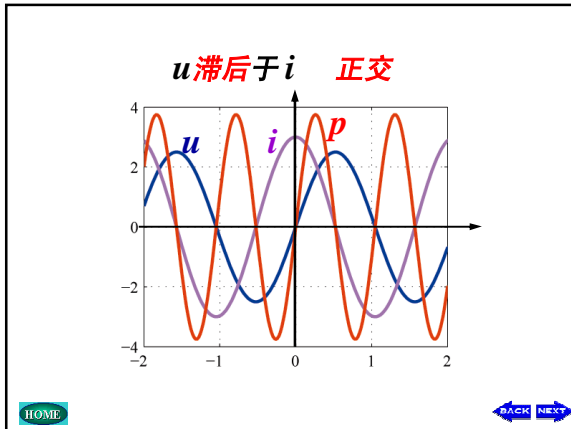

补例1 试判断下列表达式的正、误。

1. $u = \omega L \dot{I}$ ✗	5. $\frac{\dot{U}_L}{\dot{I}_L} = j\omega C$ ✗
2. $u = 5 \cos \omega t \neq 5\angle 0^\circ$	6. $\dot{I}_C = j\omega C \dot{U}_C$ ✓
3. $\dot{I}_m = j\omega C U_m$ ✗	7. $i = L \frac{du}{dt}$ ✗
4. $X_L = \frac{\dot{U}_L}{\dot{I}_L}$ ✗	

HOME BACK NEXT

补例1 试判断下列表达式的正、误。

1. $U = \omega L I$	5. $\frac{\dot{U}_L}{\dot{I}_L} = j\omega L$
2. $u = 5 \cos \omega t \neq 5\angle 0^\circ$	6. $\dot{I}_C = j\omega C \dot{U}_C$
3. $\dot{I}_m = j\omega C U_m$	7. $i = C \frac{du}{dt}$
4. $X_L = \frac{U}{I} = \frac{U_m}{I_m}$	

HOME BACK NEXT

例8-4 已知: $R=30\Omega, L=0.12H, C=12.5mF$, $i_S = 5\sqrt{2} \cos(10^3 t + 30^\circ)A$, 求电压 u_{ad} 和 u_{bd} 。

基本步骤

作相量模型 \dot{I} 求出待求量的相量 \dot{U} 求出其它量

HOME BACK NEXT

例8-4 已知: $R=30\Omega, L=0.12H, C=12.5mF$, $i_S = 5\sqrt{2} \cos(10^3 t + 30^\circ)A$, 求电压 u_{ad} 和 u_{bd} 。

解: $I_S = 5\angle 30^\circ A$

$U_R = RI = 150\angle 30^\circ V$

$U_L = j\omega LI = 600\angle 120^\circ V$

$U_C = \frac{1}{j\omega C} I = 400\angle -60^\circ V$

HOME BACK NEXT

例8-4

$U_{ad} = U_R + U_L + U_C = 250\angle 83.13^\circ V$

$U_{bd} = U_L + U_C = 200\angle 120^\circ V$

$u_{ad} = 250\sqrt{2} \cos(1000t + 83.13^\circ) V$

$u_{bd} = 200\sqrt{2} \cos(1000t + 120^\circ) V$

HOME BACK NEXT

例8-4

$$U_{ad} = (R + j\omega L + \frac{1}{j\omega C})I \quad \dot{U} = Z\dot{I}$$

$$U_{bd} = (j\omega L + \frac{1}{j\omega C})I \quad Z = |Z| \angle \varphi_Z$$

HOME BACK NEXT

选电流为参考相量作相量图
电压三角形

$$\dot{U} = \dot{U}_R + \dot{U}_L + \dot{U}_C$$

$$= \dot{U}_R + \dot{U}_X$$

HOME BACK NEXT

选电流为参考相量作相量图
电压三角形

$$\dot{U} = \dot{U}_R + \dot{U}_L + \dot{U}_C$$

$$= \dot{U}_R + \dot{U}_X$$

HOME BACK NEXT

选电流为参考相量作相量图
电压三角形

纯电感电路

$$\dot{U} = \dot{U}_R + \dot{U}_L + \dot{U}_C$$

$$= \dot{U}_R + \dot{U}_X$$
 纯电阻电路
 本题为感性电路
 纯电容电路
 容性电路

HOME BACK NEXT

例8-5 已知: $I_1=5A, I_2=20A, I_3=25A$, 求电流表A和A₄的读数。

HOME BACK NEXT

例8-5

解: 选择电压 \dot{U}_S 为参考相量

$$I_1 = 5 \angle 0^\circ A, \quad I_2 = 20 \angle -90^\circ A$$

$$I_3 = 25 \angle 90^\circ A$$

HOME BACK NEXT

例8-5

$I_4 = I_2 + I_3 = 5\angle 90^\circ \text{ A}$
 $I = I_1 + I_4 = 5 + j5 = 5\sqrt{2}\angle 45^\circ \text{ A}$

HOME BACK NEXT

选电压为参考相量作相量图

纯电容电路 I_C
 纯电感电路 I_L
 容性电路
 感性电路
 本题为容性电路
 纯电阻电路

HOME BACK NEXT

25A
 $5\sqrt{2}\text{A}$
 5A
 5A
 20A
 $q = 45^\circ$

HOME BACK NEXT

补例2 已知平衡电桥 $Z_1=1k\Omega$, $Z_2=4.2k\Omega$, $Z_3=1.43 - j0.32M\Omega$ 。求: Z_X 。

解: 平衡条件:
 $Z_1 Z_X = Z_2 Z_3$

$Z_X = \frac{Z_2 Z_3}{Z_1}$
 $= 5.99 - j1.36M\Omega$

$f = 2kHz$ 时并联参数:
 Z_3 : $1.5M\Omega$ 电阻和 $12pF$ 电容
 Z_X : $2.1M\Omega$ 电阻和 $4pF$ 电容

HOME BACK NEXT

补例3 已知 $u(t) = 120\sqrt{2} \cos(5t)$, 求: $i(t)$

相量模型

解 $U = 120\angle 0^\circ \text{ V}$
 $jX_L = j4 \cdot 5 = j20\Omega$
 $jX_C = -j \frac{1}{5 \cdot 0.02} = -j10\Omega$

HOME BACK NEXT

$$\dot{I} = \dot{I}_R + \dot{I}_L + \dot{I}_C = \frac{\dot{U}}{R} + \frac{\dot{U}}{jX_L} + \frac{\dot{U}}{jX_C}$$

$$= 120\left[\frac{1}{20} + \frac{1}{j20} - \frac{1}{j10} \right]$$

$$= 6 - j6 + j12 = 6 + j6$$

$$= 6\sqrt{2}\angle 45^\circ \text{ A}$$

$i(t) = 6\sqrt{2} \cos(5t + 45^\circ) \text{ A}$

HOME BACK NEXT