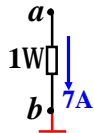


### § 3-6 结点电压法

#### 结点电位的概念:


在电路中任选一结点，设其电位为零（用⊥标记），此点称为参考点。其它各结点对参考点的电压，便是该结点的电位。记为：“ $V_x$ ”（注意：电位为单下标）。



a点电位:  $V_a = +7V$     b点电位:  $V_b = -7V$

HOME

NEXT

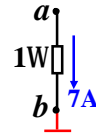

a点电位:  $V_a = +7V$     b点电位:  $V_b = -7V$

**未知量:** 指定一个参考结点，其余各个结点电位和参考结点的电位之差称为**结点电压**，用  $u_{n1}$ 、 $u_{n2}$  和  $u_{n3}$  来表示。

HOME

BACK NEXT

$$\begin{aligned} \dot{i} u_1 &= u_{n1} \\ \dot{i} u_2 &= u_{n2} \\ \dot{i} u_3 &= u_{n3} \\ \dot{i} u_4 &= u_{n1} - u_{n2} \\ \dot{i} u_5 &= u_{n2} - u_{n3} \\ \dot{i} u_6 &= u_{n1} - u_{n3} \end{aligned}$$

$$\begin{aligned} i_1 &= \frac{u_1}{R_1} - i_{S1} \\ &= \frac{u_{n1}}{R_1} - i_{S1} \\ i_2 &= \frac{u_2}{R_2} = \frac{u_{n2}}{R_2} \\ i_3 &= \frac{u_3 - u_{S3}}{R_3} \\ &= \frac{u_{n3} - u_{S3}}{R_3} \end{aligned}$$

HOME

BACK NEXT

$$\begin{aligned} i_4 &= \frac{u_4}{R_4} \\ &= \frac{u_{n1} - u_{n2}}{R_4} \\ i_5 &= \frac{u_5}{R_5} \\ &= \frac{u_{n2} - u_{n3}}{R_5} \\ i_6 &= \frac{u_6}{R_6} + i_{S6} = \frac{u_{n1} - u_{n3}}{R_6} + i_{S6} \end{aligned}$$

HOME

BACK NEXT

**KCL:**

$$\begin{aligned} i_1 + i_4 + i_6 &= 0 \\ i_2 - i_4 + i_5 &= 0 \\ i_3 - i_5 - i_6 &= 0 \end{aligned}$$

$$\begin{aligned} \dot{i} (G_1 + G_4 + G_6) u_{n1} - G_4 u_{n2} - G_6 u_{n3} &= i_{S1} - i_{S6} \\ \dot{i} -G_4 u_{n1} + (G_2 + G_4 + G_5) u_{n2} - G_5 u_{n3} &= 0 \\ \dot{i} -G_6 u_{n1} - G_5 u_{n2} + (G_3 + G_5 + G_6) u_{n3} &= i_{S6} + G_3 u_{S3} \end{aligned}$$

HOME

BACK NEXT

#### 结点方程的标准形式

$$\begin{aligned} \dot{i} G_{11} u_{n1} + G_{12} u_{n2} + G_{13} u_{n3} &= i_{S11} \\ \dot{i} G_{21} u_{n1} + G_{22} u_{n2} + G_{23} u_{n3} &= i_{S22} \\ \dot{i} G_{31} u_{n1} + G_{32} u_{n2} + G_{33} u_{n3} &= i_{S33} \end{aligned}$$

$G_{ij}$   $\dot{i} i = j$ : **自导**，第*i*个结点联结的所有支路的电导值之和(恒为正)

$\dot{i} i^1 j$ : **互导**，第*i*个结点和第*j*个结点相联的公共支路上的电导值之和取负

$i_{S11}$ 、 $i_{S22}$  等为流入各结点电流源的代数和

HOME

BACK NEXT

**补例1** 电路如图所示, 按图示结点编号列出结点电压方程。

HOME BACK NEXT

**补例1**

$$G_{11} = \frac{1}{5} + \frac{1}{2} = 0.7(S)$$

$$G_{22}$$

$$G_{33}$$

HOME BACK NEXT

**补例1**

$$G_{11} = \frac{1}{5} + \frac{1}{2} = 0.7(S)$$

$$G_{22} = \frac{1}{2} + \frac{1}{10} = 0.6(S)$$

$$G_{33}$$

HOME BACK NEXT

**补例1**

$$G_{11} = \frac{1}{5} + \frac{1}{2} = 0.7(S)$$

$$G_{22} = \frac{1}{2} + \frac{1}{10} = 0.6(S)$$

$$G_{33} = \frac{1}{10} + \frac{1}{5} = 0.3(S)$$

HOME BACK NEXT

**补例1**

$$G_{12} = G_{21} = -\frac{1}{2}(S) \quad G_{13} = G_{31} = 0$$

$$G_{23} = G_{32}$$

HOME BACK NEXT

**补例1**

$$G_{12} = G_{21} = -\frac{1}{2}(S) \quad G_{13} = G_{31} = 0$$


$$G_{23} = G_{32} = -\frac{1}{10}(S)$$

HOME BACK NEXT

$$i_{S11} = 3 - \frac{8}{2} = -1A$$

$$i_{S22} = \frac{8}{2} - 4 = 0$$


$$i_{S33} = 2A$$

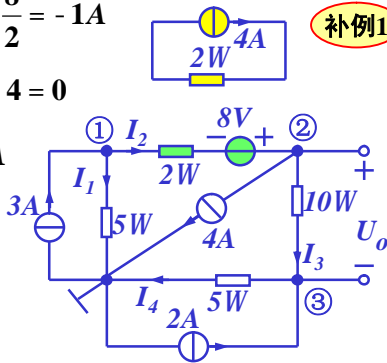

HOME

BACK NEXT

补例1

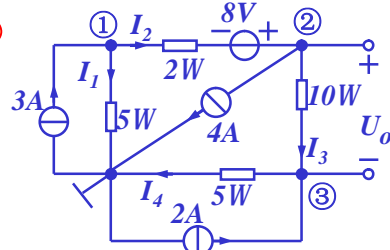


$$\dot{i} \begin{cases} 0.7u_{n1} - 0.5u_{n2} = -1 \\ \dot{i} - 0.5u_{n1} + 0.6u_{n2} - 0.1u_{n3} = 0 \\ \dot{i} - 0.1u_{n2} + 0.3u_{n3} = 2 \end{cases}$$

$$\dot{i} - 0.5u_{n1} + 0.6u_{n2} - 0.1u_{n3} = 0$$

$$\dot{i} - 0.1u_{n2} + 0.3u_{n3} = 2$$

HOME

BACK NEXT

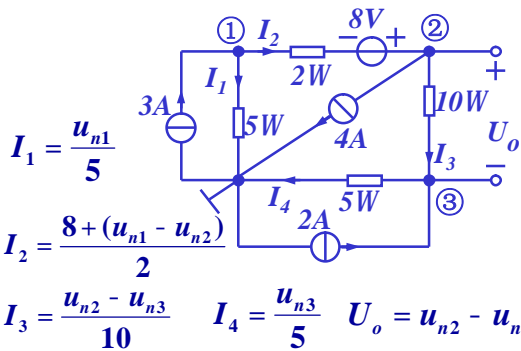

$$I_1 = \frac{u_{n1}}{5}$$


$$I_2 = \frac{8 + (u_{n1} - u_{n2})}{2}$$

$$I_3 = \frac{u_{n2} - u_{n3}}{10} \quad I_4 = \frac{u_{n3}}{5} \quad U_o = u_{n2} - u_{n3}$$

HOME

BACK NEXT

电位在电子电路中的表示法

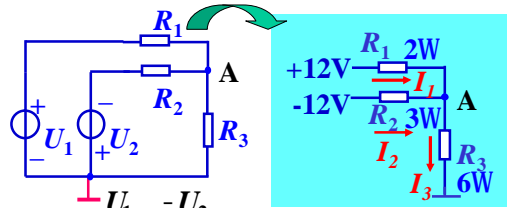


$$V_A = \frac{-U_1}{R_1} + \frac{-U_2}{R_2} + \frac{0}{R_3} = 2V$$

$$\begin{cases} I_1 = 5A \\ I_2 = -14/3A \\ I_3 = 1/3A \end{cases}$$

HOME

BACK NEXT

例3-7 列出电路的结点电压方程。

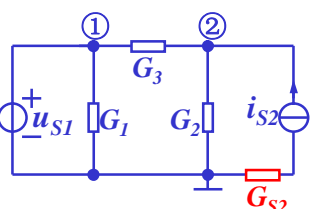


$$\begin{cases} \dot{i} u_{n1} = u_{S1} \\ \dot{i} - G_3 u_{n1} + (G_2 + G_3) u_{n2} = i_{S2} \end{cases}$$

HOME

BACK NEXT

例3-7 列出电路的结点电压方程。

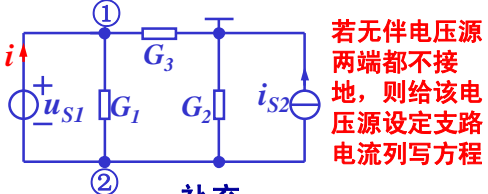

$$\text{补充: } u_{n1} - u_{n2} = u_{S1}$$

$$\dot{i} (G_1 + G_3) u_{n1} - G_1 u_{n2} = i$$

$$\dot{i} - G_1 u_{n1} + (G_1 + G_2) u_{n2} = -i - i_{S2}$$

HOME

BACK NEXT

**例3-7** 列出电路的结点电压方程。  
把 $G_1$ 当成虚元件列写方程

$i = i'?$

$$\begin{cases} \dot{u} G_3 u_{n1} = i' & \text{补充:} \\ \dot{u} G_2 u_{n2} = -i' - i_{S2} & u_{n1} - u_{n2} = u_{S1} \end{cases}$$

HOME BACK NEXT

**例3-7** 列出电路的结点电压方程。  
把 $G_1$ 当成虚元件列写方程

$$(G_2 + G_3)u_{n2} = -G_3 u_{S1} - i_{S2}$$

HOME BACK NEXT

**补例2**  
列出电路的结点电压方程。

**!!** 先把受控源看成独立源列方程，再补充控制量和未知量的关系式

HOME BACK NEXT

**补例2**  
列出电路的结点电压方程。

$$\begin{cases} \dot{u} (\frac{1}{R_1} + \frac{1}{R_2}) u_{n1} - \frac{1}{R_1} u_{n2} = i_{S1} \\ \dot{u} - \frac{1}{R_1} u_{n1} + (\frac{1}{R_1} + \frac{1}{R_3}) u_{n2} = -gu_2 - i_{S1} \end{cases}$$

补充:  $u_2 = u_{n1}$

**!!** 先把受控源看成独立源列方程，再补充控制量和未知量的关系式

HOME BACK NEXT

**补例2**  
列出电路的结点电压方程。

$$\begin{cases} \dot{u} (\frac{1}{R_1} + \frac{1}{R_2}) u_{n1} - \frac{1}{R_1} u_{n2} = i_{S1} \\ \dot{u} (g - \frac{1}{R_1}) u_{n1} + (\frac{1}{R_1} + \frac{1}{R_3}) u_{n2} = -i_{S1} \end{cases}$$

HOME BACK NEXT

**补例2**  
列出电路的结点电压方程。


$$\begin{cases} \dot{u} (\frac{1}{R_1} + \frac{1}{R_2}) u_{n1} - \frac{1}{R_1} u_{n2} = i_{S1} \\ \dot{u} u_{n2} = -i_2 \end{cases}$$

补充:  $i_2 = \frac{u_{n1}}{R_2}$

HOME BACK NEXT

补例3

列出电路的结点电压方程。

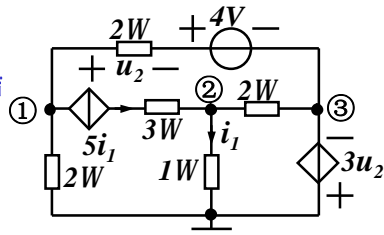

$$\begin{cases} u_{n1} - 0.5u_{n3} = 2 - 5i_1 \\ 1.5u_{n2} - 0.5u_{n3} = 5i_1 \\ u_{n3} = -3u_2 \end{cases} \quad \text{补充:} \quad \begin{cases} u_2 = u_{n1} - u_{n3} - 4 \\ i_1 = u_{n2} \end{cases}$$

HOME

BACK NEXT



注意

结点电压法: 含电压源和电阻串联支路,  
含无伴电压源,  
含受控源,  
含虚元件(和电流源串联元件)。



HOME

BACK