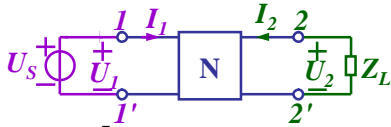


§ 16-4 二端口的转移函数

转移函数



$$H_1(s) = \frac{U_2}{U_1} \quad H_2(s) = \frac{I_2}{U_1} \quad H_3(s) = \frac{U_2}{I_1} \quad H_4(s) = \frac{I_2}{I_1}$$


$$\begin{bmatrix} \dot{U}_1 \\ \dot{U}_2 \end{bmatrix} = \begin{bmatrix} \dot{e}_{11} & \dot{e}_{12} \\ \dot{e}_{21} & \dot{e}_{22} \end{bmatrix} \begin{bmatrix} \dot{I}_1 \\ \dot{I}_2 \end{bmatrix} \Rightarrow \begin{bmatrix} \dot{e}_{11} & \dot{e}_{12} \\ \dot{e}_{21} & \dot{e}_{22} \end{bmatrix} \begin{bmatrix} \dot{U}_1 \\ \dot{U}_2 \end{bmatrix} = \begin{bmatrix} \dot{e}_{11} & \dot{e}_{12} \\ \dot{e}_{21} & \dot{e}_{22} \end{bmatrix} \begin{bmatrix} \dot{U}_1 \\ \dot{U}_2 \end{bmatrix}$$

$$Z_i = 0, \quad Z_L \text{ 任意} \quad Z_i = Z_L = 0$$

HOME

BACK NEXT

补例1 求出2-2' 端口开路 and 短路时的四个转移函数:

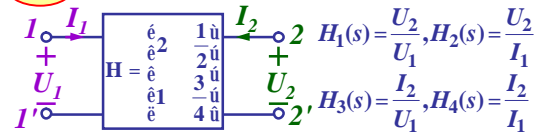

解: 2-2' 端口开路时 $I_2 = 0$ $H_3(s) = 0, H_4(s) = 0$

$$\begin{cases} U_1 = H_{11}I_1 + H_{12}U_2 \Rightarrow U_1 = -U_2 \\ I_2 = H_{21}I_1 + H_{22}U_2 = 0 \Rightarrow I_1 = -\frac{H_{22}U_2}{H_{21}} = -\frac{3U_2}{4} \end{cases}$$

$$H_1(s) = \frac{U_2}{U_1} = -1 \quad H_2(s) = \frac{U_2}{I_1} = -\frac{4}{3}$$

HOME

BACK NEXT

2-2' 端口短路时

$$U_2 = 0$$

$$H_1(s) = 0, H_2(s) = 0$$

$$\begin{cases} U_1 = H_{11}I_1 \\ I_2 = H_{21}I_1 \end{cases} \Rightarrow \begin{cases} H_3(s) = \frac{I_2}{U_1} = \frac{H_{21}}{H_{11}} = \frac{1}{2} \\ H_4(s) = \frac{I_2}{I_1} = \frac{1}{H_{21}} = 1 \end{cases}$$


End)

HOME

BACK

§ 16-5 二端口的连接

一、级联

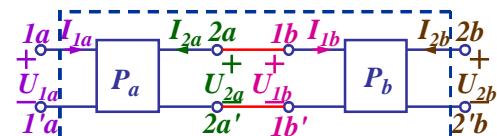


$$\begin{bmatrix} \dot{U}_{1a} \\ \dot{I}_{1a} \end{bmatrix} = \mathbf{T}_a \begin{bmatrix} \dot{U}_{2a} \\ -\dot{I}_{2a} \end{bmatrix} \quad \begin{bmatrix} \dot{U}_{1b} \\ \dot{I}_{1b} \end{bmatrix} = \mathbf{T}_b \begin{bmatrix} \dot{U}_{2b} \\ -\dot{I}_{2b} \end{bmatrix}$$

$$\begin{bmatrix} \dot{U}_1 \\ \dot{I}_1 \end{bmatrix} = \mathbf{T}_a \mathbf{T}_b \begin{bmatrix} \dot{U}_2 \\ -\dot{I}_2 \end{bmatrix} = \mathbf{T} \begin{bmatrix} \dot{U}_2 \\ -\dot{I}_2 \end{bmatrix} \quad \mathbf{T} = \mathbf{T}_a \mathbf{T}_b$$

HOME

BACK NEXT

补例1 求出图示电路的T参数矩阵

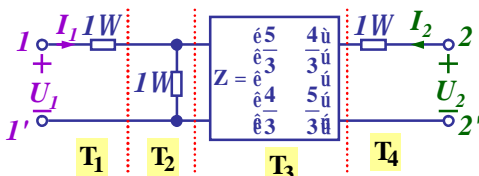

解:

$$\mathbf{T}_1 = \mathbf{T}_4 = \begin{bmatrix} \dot{e}_1 & \dot{1} \\ \dot{e}_0 & \dot{1} \end{bmatrix} \quad \mathbf{T}_2 = \begin{bmatrix} \dot{e}_1 & \dot{0} \\ \dot{e}_1 & \dot{1} \end{bmatrix}$$

HOME

BACK NEXT

$$\mathbf{T}_3 = \begin{bmatrix} \dot{e}_5 & \dot{3} \\ \dot{e}_4 & \dot{4} \\ \dot{e}_1 & \dot{3} \\ \dot{e}_2 & \dot{4} \end{bmatrix}$$

采用变换方程的方法

$$\mathbf{T} = \mathbf{T}_1 \mathbf{T}_2 \mathbf{T}_3 \mathbf{T}_4 = \begin{bmatrix} \dot{e}_{13} & \dot{6} \\ \dot{e}_4 & \dot{4} \\ \dot{e}_2 & \dot{4} \end{bmatrix}$$

$$AD - BC = 1 \quad \text{互易网络}$$

HOME

BACK NEXT

二、并联

$$\begin{bmatrix} \dot{I}_{1a} \\ \dot{I}_{2a} \end{bmatrix} = Y_1 \begin{bmatrix} \dot{U}_{1a} \\ \dot{U}_{2a} \end{bmatrix}$$

$$\begin{bmatrix} \dot{I}_{1b} \\ \dot{I}_{2b} \end{bmatrix} = Y_2 \begin{bmatrix} \dot{U}_{1b} \\ \dot{U}_{2b} \end{bmatrix}$$

$I = YU$

$Y = Y_1 + Y_2$

$$\begin{bmatrix} \dot{I}_1 \\ \dot{I}_2 \end{bmatrix} = \begin{bmatrix} \dot{I}_{1a} \\ \dot{I}_{1b} \end{bmatrix} + \begin{bmatrix} \dot{I}_{2a} \\ \dot{I}_{2b} \end{bmatrix} = (Y_1 + Y_2) \begin{bmatrix} \dot{U}_1 \\ \dot{U}_2 \end{bmatrix}$$

HOME BACK NEXT

补例2 求出图示电路的Y参数矩阵, 并作p型等效电路

解: **$Y = Y_1 + Y_2$**

HOME BACK NEXT

$$Z_1 = \begin{bmatrix} 8 & 6 \\ 6 & 8 \end{bmatrix} \quad Y_1 = Z_1^{-1} = \frac{1}{28} \begin{bmatrix} 8 & -6 \\ -6 & 8 \end{bmatrix}$$

$$Y_2 = \begin{bmatrix} \frac{1}{4} & -\frac{1}{4} \\ \frac{1}{4} & \frac{1}{4} \end{bmatrix} \quad Y = Y_1 + Y_2 = \begin{bmatrix} \frac{15}{28} & -\frac{13}{28} \\ \frac{13}{28} & \frac{15}{28} \end{bmatrix} (S)$$

$Y_{12} = Y_{21}$ & $Y_{11} = Y_{22}$ 网络对称

HOME BACK NEXT

HOME BACK NEXT

三、串联

$$\begin{bmatrix} \dot{U}_{1a} \\ \dot{U}_{2a} \end{bmatrix} = Z_1 \begin{bmatrix} \dot{I}_{1a} \\ \dot{I}_{2a} \end{bmatrix}$$

$$\begin{bmatrix} \dot{U}_{1b} \\ \dot{U}_{2b} \end{bmatrix} = Z_2 \begin{bmatrix} \dot{I}_{1b} \\ \dot{I}_{2b} \end{bmatrix}$$

$U = ZI$

$Z = Z_1 + Z_2$

$$\begin{bmatrix} \dot{U}_1 \\ \dot{U}_2 \end{bmatrix} = \begin{bmatrix} \dot{U}_{1a} \\ \dot{U}_{1b} \end{bmatrix} + \begin{bmatrix} \dot{U}_{2a} \\ \dot{U}_{2b} \end{bmatrix} = (Z_1 + Z_2) \begin{bmatrix} \dot{I}_1 \\ \dot{I}_2 \end{bmatrix}$$

HOME BACK NEXT


补例3 求出图示电路的Z参数矩阵, 并作T型等效电路

解:
$$Y_1 = \begin{bmatrix} \frac{3}{4} & -\frac{1}{4} \\ \frac{1}{4} & \frac{3}{4} \end{bmatrix}$$

$$Z_1 = Y_1^{-1} = \frac{1}{2} \begin{bmatrix} 3 & 1 \\ 1 & 3 \end{bmatrix}$$

$$Z_2 = \begin{bmatrix} 6 & 6 \\ 6 & 6 \end{bmatrix} \quad Z = Z_1 + Z_2 = \frac{1}{2} \begin{bmatrix} 15 & 13 \\ 13 & 15 \end{bmatrix} (W)$$

HOME BACK NEXT

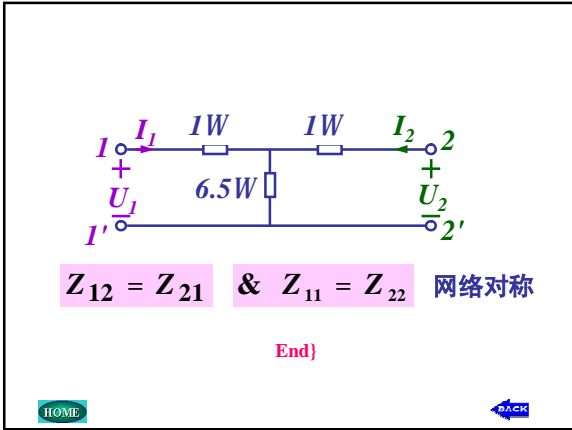

§ 16-6 回转器和负阻抗变换器

一、阻抗变换

T参数方程:

$$\begin{cases} \dot{U}_1 = \dot{A}U_2 + \dot{B}(-I_2) \\ \dot{I}_1 = \dot{C}U_2 + \dot{D}(-I_2) \end{cases}$$

$$Z_i = \frac{U_1}{I_1} = \frac{AU_2 + B(-I_2)}{CU_2 + D(-I_2)} = \frac{A(-Z_L I_2) + B(-I_2)}{C(-Z_L I_2) + D(-I_2)} = \frac{AZ_L + B}{CZ_L + D}$$

2-2' 外特性方程:

$$U_2 = -Z_L I_2$$

二、几种特殊二端口网络

1、回转器:

$$Z_i = \frac{AZ_L + B}{CZ_L + D} = \frac{0 \times Z_L + r}{1 \times Z_L + 0} = \frac{r^2}{Z_L} = \frac{1}{g^2 Z_L}$$

$$T = \begin{pmatrix} \dot{e} & 1 \\ \dot{e} & 0 \end{pmatrix} \begin{pmatrix} \dot{u} \\ \dot{u} \end{pmatrix} = \begin{pmatrix} \dot{e} & 0 \\ \dot{e} & g \end{pmatrix} \begin{pmatrix} \dot{u} \\ \dot{u} \end{pmatrix}$$

$$T = \begin{pmatrix} \dot{e} & 0 \\ \dot{e} & r \end{pmatrix} \begin{pmatrix} \dot{u} \\ \dot{u} \end{pmatrix} = \begin{pmatrix} \dot{e} & 1 \\ \dot{e} & r \end{pmatrix} \begin{pmatrix} \dot{u} \\ \dot{u} \end{pmatrix}$$

2、负阻抗变换器:

$$T = \begin{pmatrix} \dot{e} - k & 0 \\ \dot{e} & 1 \end{pmatrix} \begin{pmatrix} \dot{u} \\ \dot{u} \end{pmatrix}$$

$$Z_i = \frac{AZ_L + B}{CZ_L + D} = \frac{-kZ_L + 0}{0 \times Z_L + 1} = -kZ_L$$

2、负阻抗变换器:

$$T = \begin{pmatrix} \dot{e} & 1 \\ \dot{e} & 0 \end{pmatrix} \begin{pmatrix} \dot{u} \\ \dot{u} \end{pmatrix} = \begin{pmatrix} \dot{e} & 1 \\ \dot{e} & -k \end{pmatrix} \begin{pmatrix} \dot{u} \\ \dot{u} \end{pmatrix}$$

$$Z_i = \frac{AZ_L + B}{CZ_L + D} = \frac{Z_L + 0}{0 \times Z_L + (-k)} = -\frac{1}{k} Z_L$$

运放电路模拟负阻抗变换器 (INIC)

由“虚短”: $U_1 = U_2$ 由“虚断”: $I_+ = I_- = 0$

$$I_1 = -\frac{R_2}{R_1} (-I_2)$$

$$I_1 R_1 = I_2 R_2$$

运放电路模拟
负阻抗变换器
(INIC)

$$T = \begin{bmatrix} 1 & 0 \\ 0 & -k \end{bmatrix}$$

HOME BACK NEXT

三、特征阻抗

$A = D \quad Z_i = Z_L = Z_C$

特征阻抗

$$Z_C = \frac{AZ_C + B}{CZ_C + D}$$

$$\Rightarrow Z_C = \sqrt{\frac{B}{C}}$$

HOME BACK NEXT

补例 $R=2W, n=2, X_{L1}=4W, X_{C1}=-1W, X_{L2}=2W$, 求入端等效复阻抗 $Z_i=?$

解:

$$T_1 = \begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix} \quad T_2 = \begin{bmatrix} 1 & 0 \\ 1 & j4 \end{bmatrix} \quad T_3 = \begin{bmatrix} 2 & 0 \\ 0 & 1 \end{bmatrix} \quad T_4 = \begin{bmatrix} 1 & -j1 \\ 0 & 1 \end{bmatrix}$$

HOME BACK NEXT

$$T = T_1 T_2 T_3 T_4 = \begin{bmatrix} 2-j1 & -j2 \\ 1 & 0 \end{bmatrix}$$

$$Z_i = \frac{AZ_L + B}{CZ_L + D} = \frac{(2-j1) \times j2 - j2}{-j\frac{1}{2} \times j2 + 0} = 2 + j2 W$$

HOME BACK NEXT

End)

$$Z_i = 2 + j2 W$$

HOME BACK