

第十六章 二端口网络

- § 16-1 二端口网络
- § 16-2 二端口的方程和参数
- § 16-3 二端口的等效电路
- § 16-4 二端口的转移函数
- § 16-5 二端口的连接
- § 16-6 回转器和负阻抗变换器

HOME

NEXT


本章重点:

- 二端口网络四种参数方程及参数矩阵的求解。
- 二端口网络的等效电路。
- 二端口网络的级联及其参数的求解。
- 二端口网络的转移函数和阻抗变换。

End

BACK

§ 16-1 二端口网络

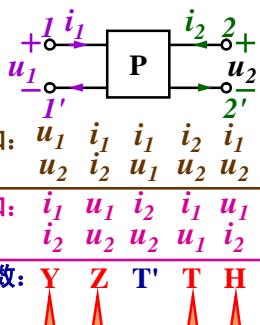


已知: $u_1, i_1, i_2, i_1', i_2', i_1, i_2$
未知: $i_1, u_1, i_2, i_1, u_1, i_2, i_1$

对应参数: Y, Z, T', T, H, G

HOME

NEXT


学习过的二端口元件:

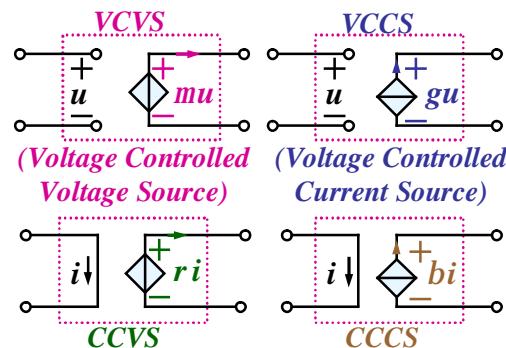

HOME

BACK NEXT

学习过的二端口元件:

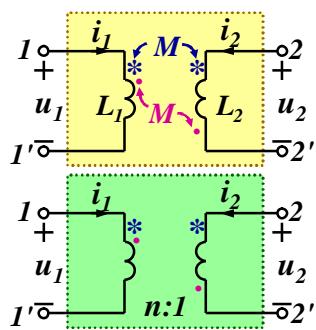


End

§ 16-2 二端口的方程和参数

一、Y参数

叠加定理:

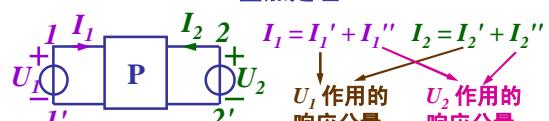

Y参数 $\begin{cases} I_1 = Y_{11} U_1 + Y_{12} U_2 \\ I_2 = Y_{21} U_1 + Y_{22} U_2 \end{cases}$

Y参数矩阵: $\mathbf{Y} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$

$$\begin{aligned} \hat{\mathbf{I}}_1 &= \hat{Y}_{11} Y_{12} \hat{\mathbf{U}}_1 \\ \hat{\mathbf{I}}_2 &= \hat{Y}_{21} Y_{22} \hat{\mathbf{U}}_2 \end{aligned}$$

I = YU

HOME

NEXT

$$Y_{11} = \left. \frac{I_1}{U_1} \right|_{U_2=0} \quad Y_{21} = \left. \frac{I_2}{U_1} \right|_{U_2=0}$$

$$Y_{12} = \left. \frac{I_1}{U_2} \right|_{U_1=0} \quad Y_{22} = \left. \frac{I_2}{U_2} \right|_{U_1=0}$$

短路导纳矩阵

若P不含受控源 $Y_{12} = Y_{21}$ **三个独立参数**

& $Y_{11} = Y_{22}$

若P电气对称 **两个独立参数**

◀ BACK ▶ NEXT

HOME

补例1 求出图示电路的Y参数矩阵

◀ BACK ▶ NEXT

HOME

补例1 求出图示电路的Y参数矩阵

解: $Y_{11} = \left. \frac{I_1}{U_1} \right|_{U_2=0} = \frac{0.5U_1 - 0.5U_R}{U_1} = 2S$

$Y_{21} = \left. \frac{I_2}{U_1} \right|_{U_2=0} = \frac{0.5U_R}{U_1} = -1.5S$

◀ BACK ▶ NEXT

HOME

$Y_{12} = \left. \frac{I_1}{U_2} \right|_{U_1=0} = \frac{-3U_2 - 0.5U_R}{U_2} = -3.5S$

$Y_{22} = \left. \frac{I_2}{U_2} \right|_{U_1=0} = \frac{U_2 + 0.5U_R}{U_2} = 1.5S$

$$Y = \begin{bmatrix} 2 & -3.5 \\ -1.5 & 1.5 \end{bmatrix}$$

◀ BACK ▶ NEXT

HOME

可列写结点方程求Y参数矩阵 (电路只有两个独立结点)

$\frac{1}{2}(0.5 + 0.5)U_1 - 0.5U_2 = I_1 + 3U_2 - U_1$

$\frac{1}{2} - 0.5U_1 + (1 + 0.5)U_2 = I_2 + U_1$

$$\begin{cases} \frac{1}{2}2U_1 - 3.5U_2 = I_1 \\ \frac{1}{2} - 1.5U_1 + 1.5U_2 = I_2 \end{cases}$$

$YU = I$

◀ BACK ▶ NEXT

HOME

二、Z参数

Z参数方程

$$\begin{cases} U_1 = Z_{11}I_1 + Z_{12}I_2 \\ U_2 = Z_{21}I_1 + Z_{22}I_2 \end{cases}$$

Z参数矩阵:

$Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$

$$\begin{cases} eU_1 = eZ_{11}Z_{12} \bar{e}I_1 \bar{e} \\ eU_2 = eZ_{21}Z_{22} \bar{e}I_2 \bar{e} \end{cases}$$

$U = ZI \quad I = YU \quad P \quad Z = Y^{-1}$

◀ BACK ▶ NEXT

HOME

$$Z_{11} = \frac{U_1}{I_1} \Big|_{I_2=0}, Z_{21} = \frac{U_2}{I_1} \Big|_{I_2=0}$$

$$Z_{12} = \frac{U_1}{I_2} \Big|_{I_1=0}, Z_{22} = \frac{U_2}{I_2} \Big|_{I_1=0}$$

开路阻抗矩阵

若P不含受控源 $Z_{12} = Z_{21}$ 网络互易


& $Z_{11} = Z_{22}$ 三个独立参数

若P电气对称 两个独立参数

[HOME](#)

[BACK](#) [NEXT](#)

补例2 求出图示正弦稳态电路的Z参数矩阵

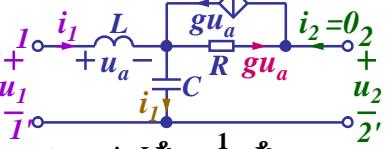

$$Z_{11} = \frac{\mathbf{U}_1}{\mathbf{I}_1} \Big|_{\mathbf{I}_2=0} = \frac{jwL\mathbf{I}_1 + \frac{1}{jwC}\mathbf{I}_1}{\mathbf{I}_1} = jwL + \frac{1}{jwC}$$

$$Z_{21} = \frac{\mathbf{U}_2}{\mathbf{I}_1} \Big|_{\mathbf{I}_2=0} = \frac{-R \times g \mathbf{U}_a + \frac{1}{jwC}\mathbf{I}_1}{\mathbf{I}_1} = -jwLRg + \frac{1}{jwC}$$

[HOME](#)

[BACK](#) [NEXT](#)

$$Z_{12} = \frac{\mathbf{U}_1}{\mathbf{I}_2} \Big|_{\mathbf{I}_1=0} = \frac{\frac{1}{jwC}\mathbf{I}_2}{\mathbf{I}_2} = \frac{1}{jwC} \quad Z = \begin{vmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix}$$

$$Z_{22} = \frac{\mathbf{U}_2}{\mathbf{I}_2} \Big|_{\mathbf{I}_1=0} = \frac{R\mathbf{I}_2 + \frac{1}{jwC}\mathbf{I}_2}{\mathbf{I}_2} = R + \frac{1}{jwC}$$

[HOME](#)

[BACK](#) [NEXT](#)

可列写回路方程求Z参数矩阵 (电路只有两个独立回路)

$$(jwL + \frac{1}{jwC})\mathbf{I}_1 + \frac{1}{jwC}\mathbf{I}_2 = \mathbf{U}_1$$

$$\frac{1}{jwC}\mathbf{I}_1 + (R + \frac{1}{jwC})\mathbf{I}_2 = \mathbf{U}_2 + Rg\mathbf{U}_a$$

$$\mathbf{U}_a = jwL\mathbf{I}_1$$

[HOME](#)

[BACK](#) [NEXT](#)

可列写回路方程求Z参数矩阵 (电路只有两个独立回路)

$$\frac{(jwL + \frac{1}{jwC})\mathbf{I}_1}{jwC} + \frac{1}{jwC}\mathbf{I}_2 = \mathbf{U}_1$$

$$(-jwLRg + \frac{1}{jwC})\mathbf{I}_1 + (R + \frac{1}{jwC})\mathbf{I}_2 = \mathbf{U}_2$$

$$\mathbf{ZI} = \mathbf{U}$$

[HOME](#)

[BACK](#) [NEXT](#)

三、T参数(传输参数, A参数)

$$\begin{cases} U_1 = A U_2 + B (-I_2) \\ I_1 = C U_2 + D (-I_2) \end{cases}$$

$$\begin{cases} U_1 = Y_{11} U_1 + Y_{12} U_2 \\ I_2 = Y_{21} U_1 + Y_{22} U_2 \end{cases}$$

$$\begin{cases} U_1 = -\frac{Y_{22}}{Y_{21}} U_2 + \frac{1}{Y_{21}} I_2 \\ I_1 = (Y_{12} - \frac{Y_{11} Y_{22}}{Y_{21}}) U_2 + \frac{Y_{11}}{Y_{21}} I_2 \end{cases}$$

$$T = \begin{bmatrix} \frac{Y_{22}}{Y_{21}} & -\frac{1}{Y_{21}} \\ \frac{Y_{12}}{Y_{21}} - \frac{Y_{11} Y_{22}}{Y_{21}} & \frac{Y_{11}}{Y_{21}} \end{bmatrix}$$

[HOME](#)

[BACK](#) [NEXT](#)

$A = \frac{U_1}{U_2} \Big|_{I_2=0}$ $B = \frac{U_1}{-I_2} \Big|_{U_2=0}$
 $C = \frac{I_1}{U_2} \Big|_{I_2=0}$ $D = \frac{I_1}{-I_2} \Big|_{U_2=0}$

网络互易 $B = C$ $Y_{12} = Y_{21}$
 $AD - BC = \frac{Y_{11}Y_{22}}{Y_{21}^2} - (\frac{Y_{11}Y_{22}}{Y_{21}^2} - \frac{Y_{12}}{Y_{21}}) = \frac{Y_{12}}{Y_{21}}$
 $AD - BC = 1$
网络对称 $\& Y_{11} = Y_{22}$ $\& A = D$

[HOME](#) [BACK](#) [NEXT](#)

补例3 求出图示电路的T参数矩阵

解: $A = \frac{U_1}{U_2} \Big|_{I_2=0} = 2.5$ $C = \frac{I_1}{U_2} \Big|_{I_2=0} = \frac{1}{20}$
 $I_1 = \frac{1}{30} + \frac{1}{60} = \frac{1}{20}$ $U_1 = 10I_1 + 2U_2 = 2.5$

[HOME](#) [BACK](#) [NEXT](#)

$B = \frac{U_1}{-I_2} \Big|_{U_2=0} = 40$ $D = \frac{I_1}{-I_2} \Big|_{U_2=0} = 1$
 $U_1 = -40I_2 = 40$ $T = \begin{pmatrix} 2.5 & 40 \\ 1/20 & 1 \end{pmatrix}$
 $I_1 = -I_2 = 1$

[HOME](#) [BACK](#) [NEXT](#)

简单二端口
网络的参数

Y不存在
 $Z = \begin{pmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{pmatrix}$
 $T = \begin{pmatrix} 1 & Z_{12} \\ 0 & 1 \end{pmatrix}$

[HOME](#) [BACK](#) [NEXT](#)

简单二端口
网络的参数

Z不存在
 $Y = \begin{pmatrix} 1/Z_{11} & -1/Z_{12} \\ -1/Z_{21} & 1/Z_{22} \end{pmatrix}$
 $T = \begin{pmatrix} 1 & Z_{12} \\ 0 & 1 \end{pmatrix}$

[HOME](#) [BACK](#) [NEXT](#)

四、H参数

H参数方程
 $\begin{cases} U_1 = H_{11}I_1 + H_{12}U_2 \\ I_2 = H_{21}I_1 + H_{22}U_2 \\ I_1 = Y_{11}U_1 + Y_{12}U_2 \\ I_2 = Y_{21}U_1 + Y_{22}U_2 \end{cases}$
 $\begin{cases} U_1 = \frac{1}{Y_{11}}I_1 - \frac{Y_{12}}{Y_{11}}U_2 \\ I_2 = \frac{Y_{21}}{Y_{11}}I_1 + (Y_{22} - \frac{Y_{12}Y_{21}}{Y_{11}})U_2 \end{cases}$

H参数矩阵
 $H = \begin{pmatrix} 1/Y_{11} & -Y_{12}/Y_{11} \\ Y_{21}/Y_{11} & Y_{22} - Y_{12}Y_{21}/Y_{11} \end{pmatrix}$

[HOME](#) [BACK](#) [NEXT](#)

